

# **The Ins and Outs of Audio Transformers**

**How to Choose them and  
How to Use them**

# **Steve Hogan**

**Product Development Engineer, Jensen Transformers**  
1983 – 1989

Designed new products and  
provided application assistance to Customers

**VP Engineering, Jensen Transformers**  
1989-2003

Re-designed entire product line from JE-xxx to JT-xxx  
using computer-controlled winding equipment and  
improved materials and methods

# Audio Transformer Basics

- Audio Transformer is a device consisting of a (driven) primary winding wound around a core of magnetic material.
- One or more secondary windings wound around the same core.
- AC Voltage on the primary creates a changing magnetic flux in the core.
- Changing magnetic flux in the core generates a signal in the secondary winding(s).
- Signals can be sent from the primary side to the secondary side without any direct connection since they are magnetically coupled.

# Galvanic Isolation

- Audio Transformers allow one to connect two pieces of equipment together “without connecting them together”.
- No direct contact between primary and secondary windings allows each winding to be at a different DC potential. Phantom power causes the mic primary to be +48V higher than the secondary.
- Transformers can break “Ground Loops” and solve “Pin 1 Problems”

# Voltage Transformation

- Transformers can step the secondary voltage up or down relative to the primary voltage.
- Voltage change = Ratio of primary turns and secondary turns.
- **$V_{pri}/V_{sec} = N_{pri}/N_{sec}$**
- Power (Volts x Amps) is same on both sides.

# Voltage and Current Relationships

- 10V @ 10mA 1:1 turns ratio = 10V @ 10mA
- 10V @ 10mA 1:10 turns ratio = 100V @ 1mA
- 10V @ 10mA 10:1 turns ratio = 1V @ 100mA

# Source and Load Impedance

- Load  $Z$  is the load placed on the secondary winding(s). It may be resistive only, or it may be complex with capacitive or inductive reactance.
- For example a passive equalizer with an input  $Z$  of 600 Ohms will present a 600 Ohm load  $Z$  to the secondary of an input transformer placed in front of it.
- Source  $Z$  is the impedance in series with the voltage produced by the device driving the primary winding.
- For example, a Shoeps mic with 12 Ohms output  $Z$  has a source  $Z$  of 12 Ohms to the transformer primary.

# Impedance Transformation

- Impedance is changed in BOTH DIRECTIONS.
- $Z_{pri}/Z_{sec} = (N_{pri}/N_{sec})^2$
- Step-up allows low Z sources (microphones) to match amplifier noise characteristics for lowest noise
- Step-down allows vacuum tubes to drive low Z speaker loads.



# Impedance Relationships

- 150 Ohm Mic    1:10 turns ratio    150k load resistor
- Voltage ratio is 1:10, Impedance ratio is 1:100 ( $10^2$ )
- Microphone sees a  $150K / 100 = 1K5$  Load Z
- Amplifier sees  $150 \text{ Ohm mic} * 100 = 15K$  as a source.
- Above calculations do not include winding resistances.

# Leakage L (Inductance)

- An inductor is an electronic component that opposes the change in current through the device. Its reactance (measured in Ohms) increases with increasing frequency.
- Leakage Inductance is a parasitic series inductance in series with the transformer. It is caused by incomplete magnetic coupling of the primary winding to the secondary winding(s).
- It can affect the frequency and transient response of the transformer when the secondary has capacitive loading (like driving a long cable).

# Faraday Shields

- Copper Foil Shield between primary and secondary layers in the transformer assembly.
- Greatly reduces capacitive coupling between primary and secondary, thus giving the transformer excellent common-mode rejection.
- Used in input transformers.

# Input Transformer



# Input Transformers

- Input transformer primary must be fed from various devices with various source impedances not under control of the user.
- Input transformer secondary can be loaded as required for best performance, since user/designer has control of the load.
- Input types typically use multiple interleaved layers of primary and secondary to reduce Leakage L, and Faraday shields to provide inputs that are capacitively balanced with respect to ground.
- Input transformers have excellent CMRR.


# Using Input Transformers

- Input type faraday shielded transformer has excellent CMRR.
- Input transformers have limited bandwidth and are good at rejecting out-of-band unwanted signals like RFI.
- Balanced primary can be reversed to obtain polarity reversal.
- Steps should be taken to eliminate any DC on Primary, since DC will increase THD and reduce headroom.

# Output Transformer



# Output Transformer

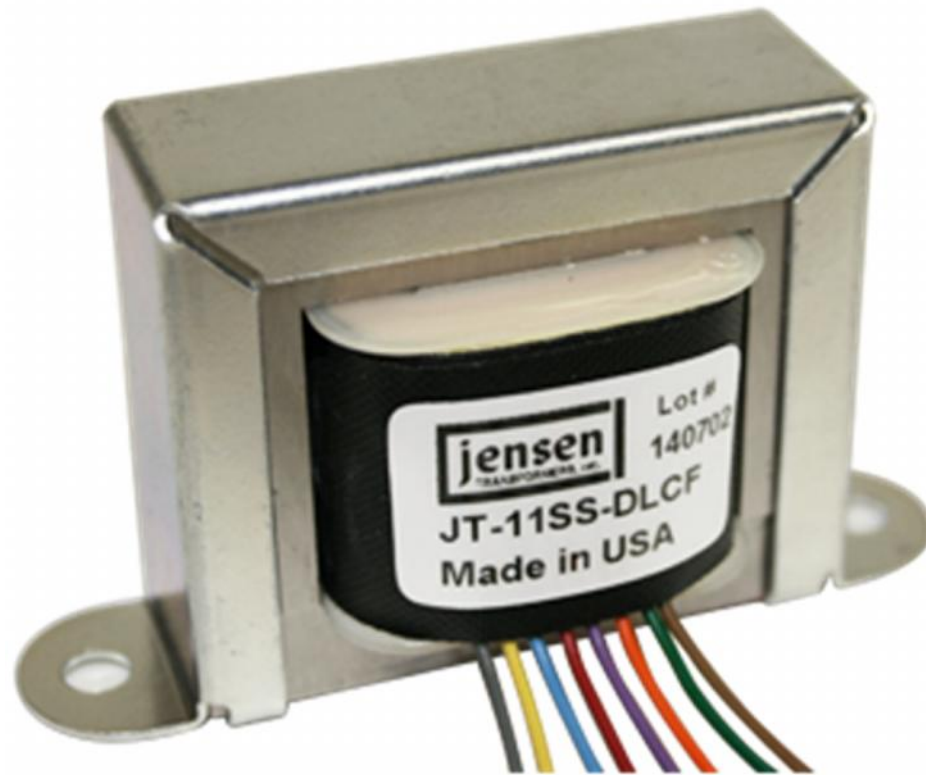



# Output Transformers


- Output transformer primaries are typically driven by line driver amplifier stages controlled by the user/designer.
- Output transformer secondaries must drive long cables or short cables, no load or heavy load with no load induced frequency response or transient errors.
- Typically they are wound multifilar for minimal Leakage L. They have very high winding to winding capacitance, however.

## Bifilar Wound Output Transformer

Primary wire wound simultaneously side-by-side with secondary wire.

Almost all magnetic flux generated by the primary is “caught” by the secondary wire right next to it.

Winding to winding capacitance is high.

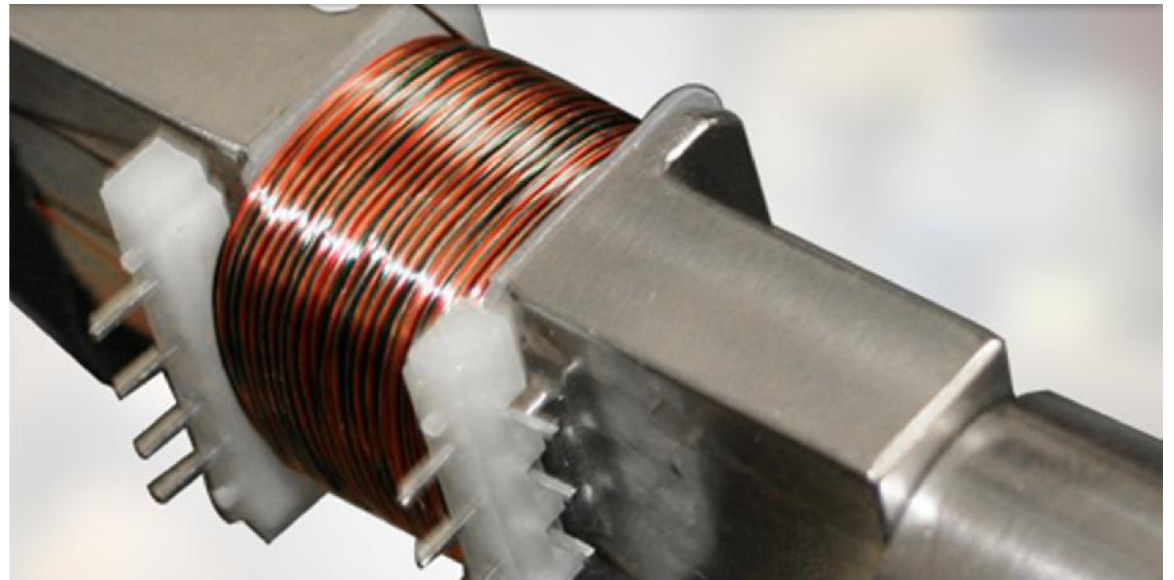

# Using Output Transformers

- Large capacitance between windings needs some precautions: Do not use an output transformer to reverse polarity. It puts a huge capacitive load on the line driver amplifier.
- For symmetrical drive, feed from bridge amp.
- Driving primary from single-ended amplifier allows excellent performance into both Balanced and Unbalanced Loads.
- Drive primary from very DC coupled amplifier with low output Z. DC servo is recommended to eliminate offsets.
- If you must capacitively couple to primary, use very large (>470uF) cap, to reduce sub-sonic resonance peak.


# Transformer Distortion

- Transformer THD is 3d harmonic until saturation. Musically related (octave + fifth).
- Transformer THD is a Low Frequency Problem.
- THD diminishes 6 dB per octave.
- Intermodulation Distortion is negligible in transformers.
- THD caused by Source Z (including primary resistance) being shunted by non-linear primary inductance.

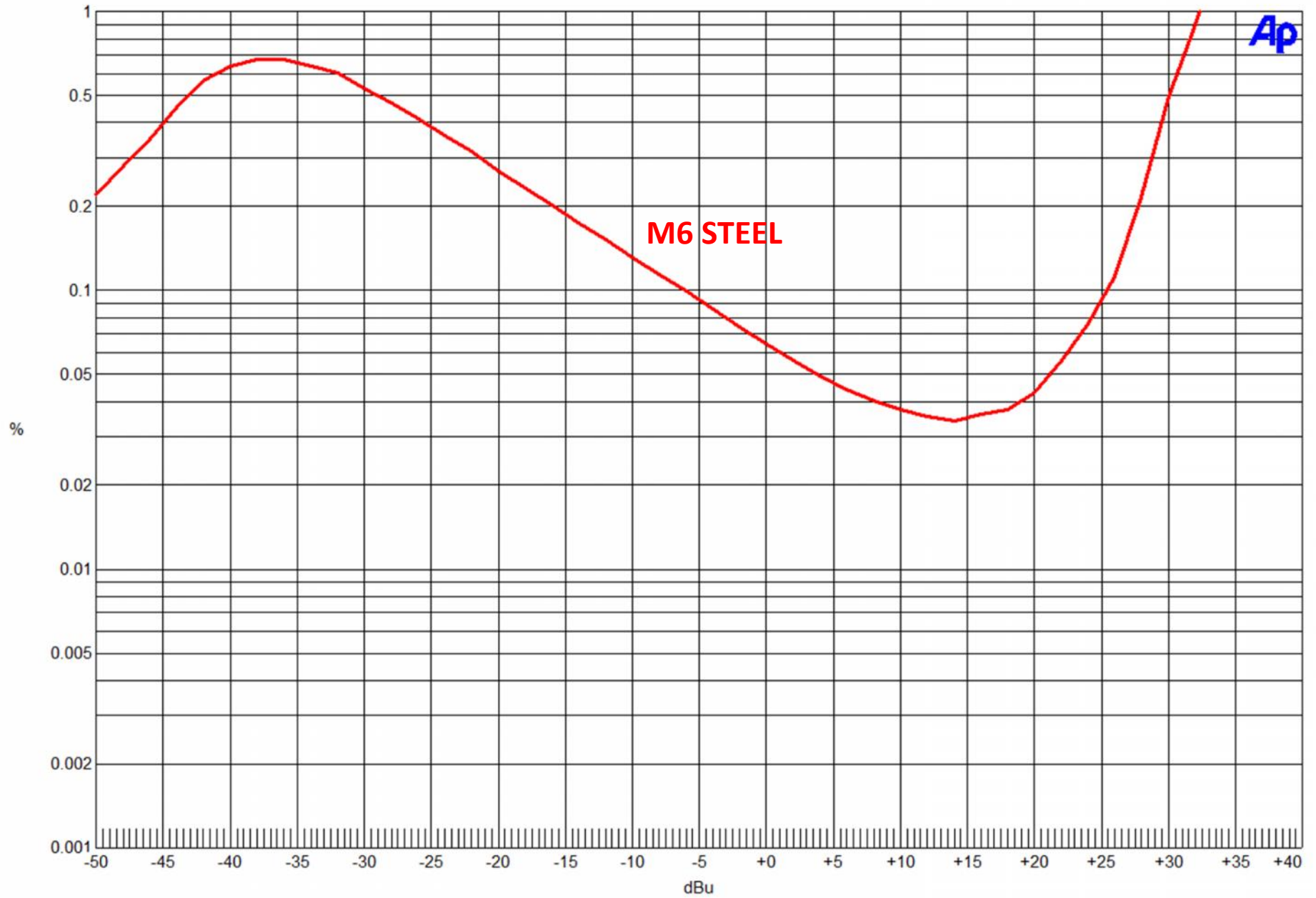
# Types of Core Material

- Three commonly used types of core material used in audio transformers:
- M6 grain-oriented silicon steel: Used in output transformers, especially vacuum tube output.
- 50% nickel alloy: Used in “sound reinforcement” grade output transformers.
- 80% nickel alloy: Used in “recording studio” grade output transformers and all input transformers. Handles less maximum level, but is much more linear than the others.


JT-11-D (M6 Steel), JT-11-DL (50% NI), JT-11-DM (80% NI) 20 Hz THD vs LEVEL,  $R_s = 0$  Ohm



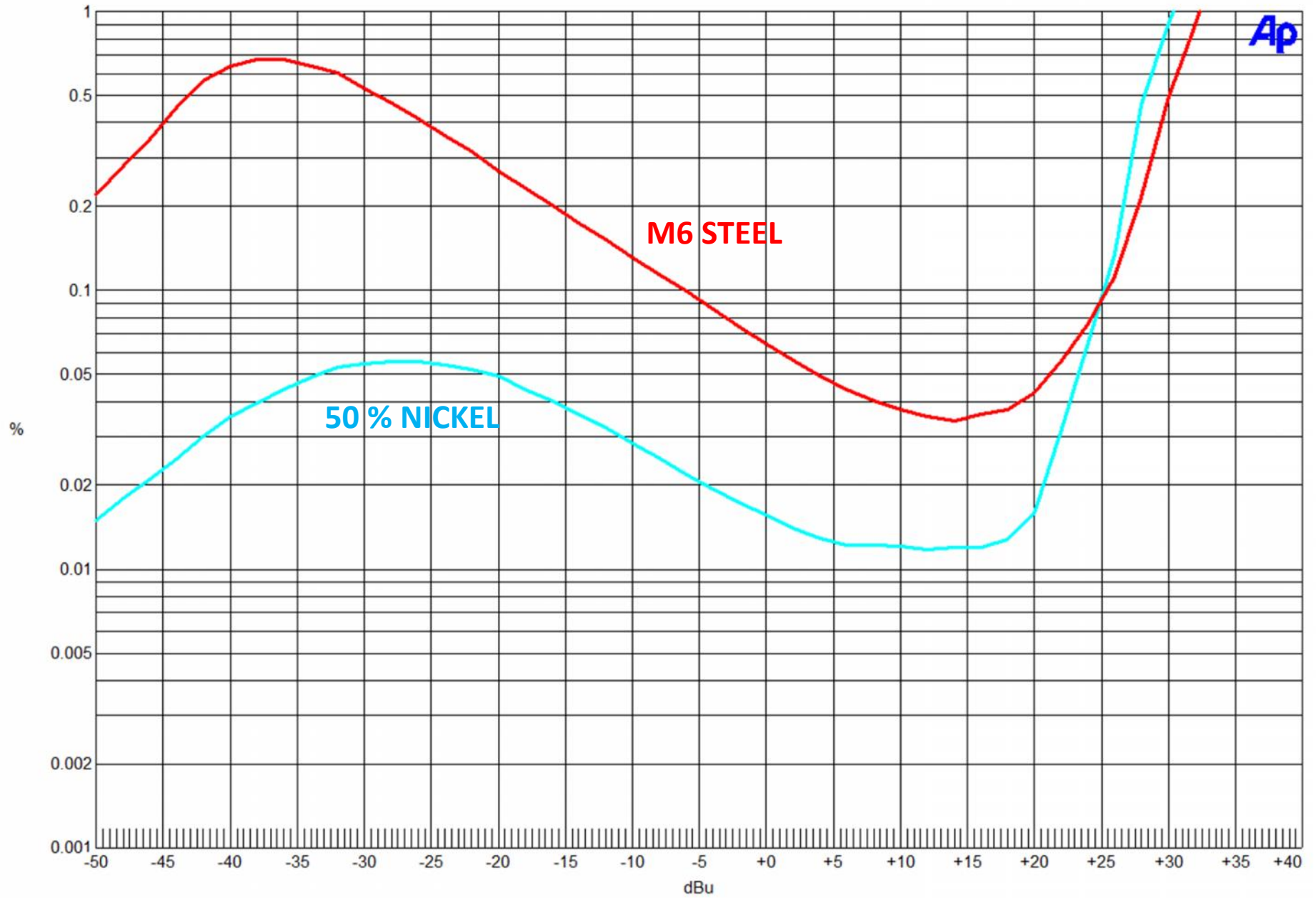JT-11-D (M6 Steel), JT-11-DL (50% NI), JT-11-DM (80% NI) 20 Hz THD vs LEVEL,  $R_s = 0 \text{ Ohm}$



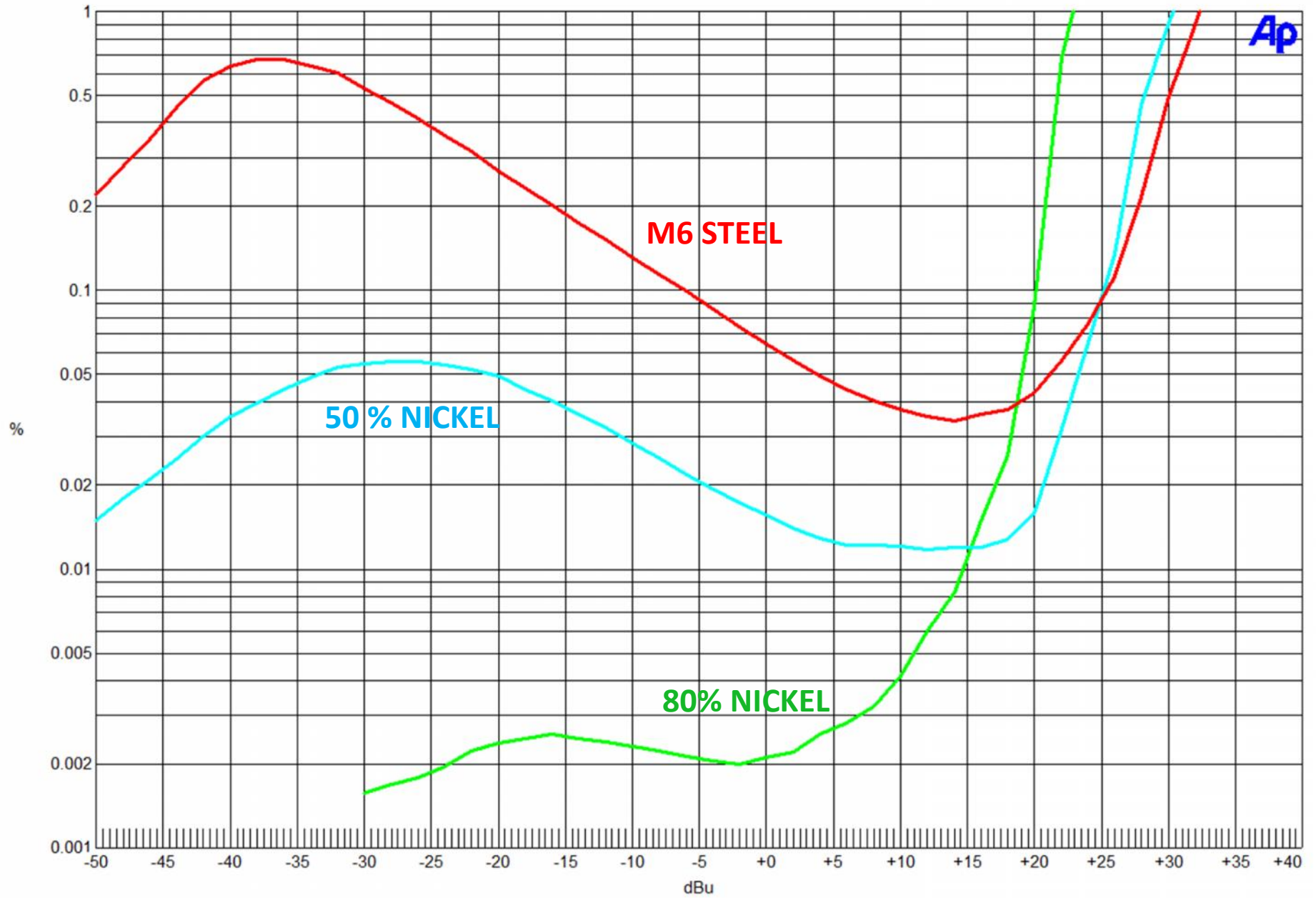JT-11-D (M6 Steel), JT-11-DL (50% NI), JT-11-DM (80% NI) 20 Hz THD vs LEVEL,  $R_s = 0$  Ohm




Ap




- THD decreases with increasing frequency.
- Maximum Level Increases with increasing frequency.
- Following graphs show THD at various frequencies.

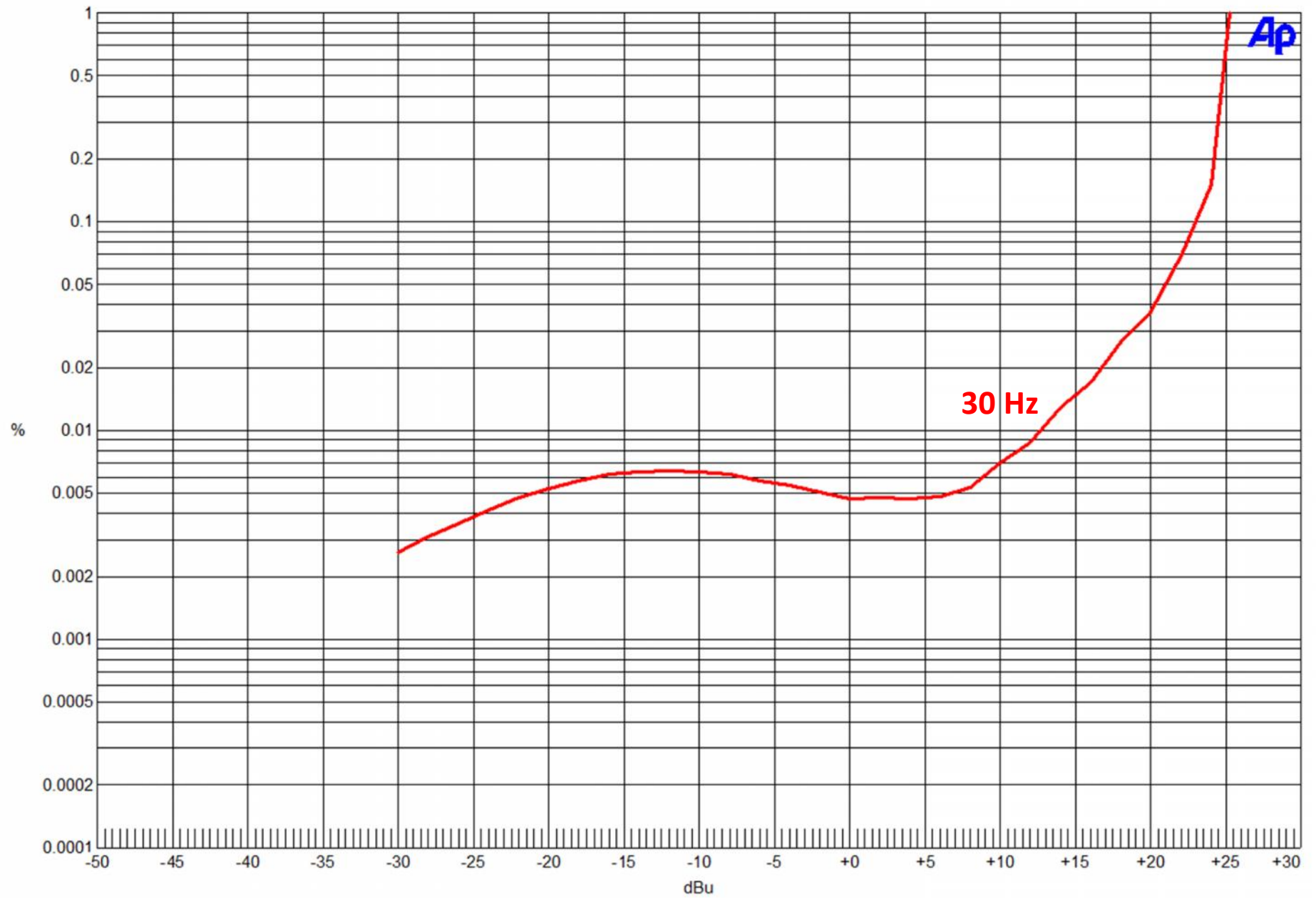
JT-11-DM (HN) THD vs FREQUENCY: F = 30Hz, 50Hz, 100Hz, Rs = 150 Ohms



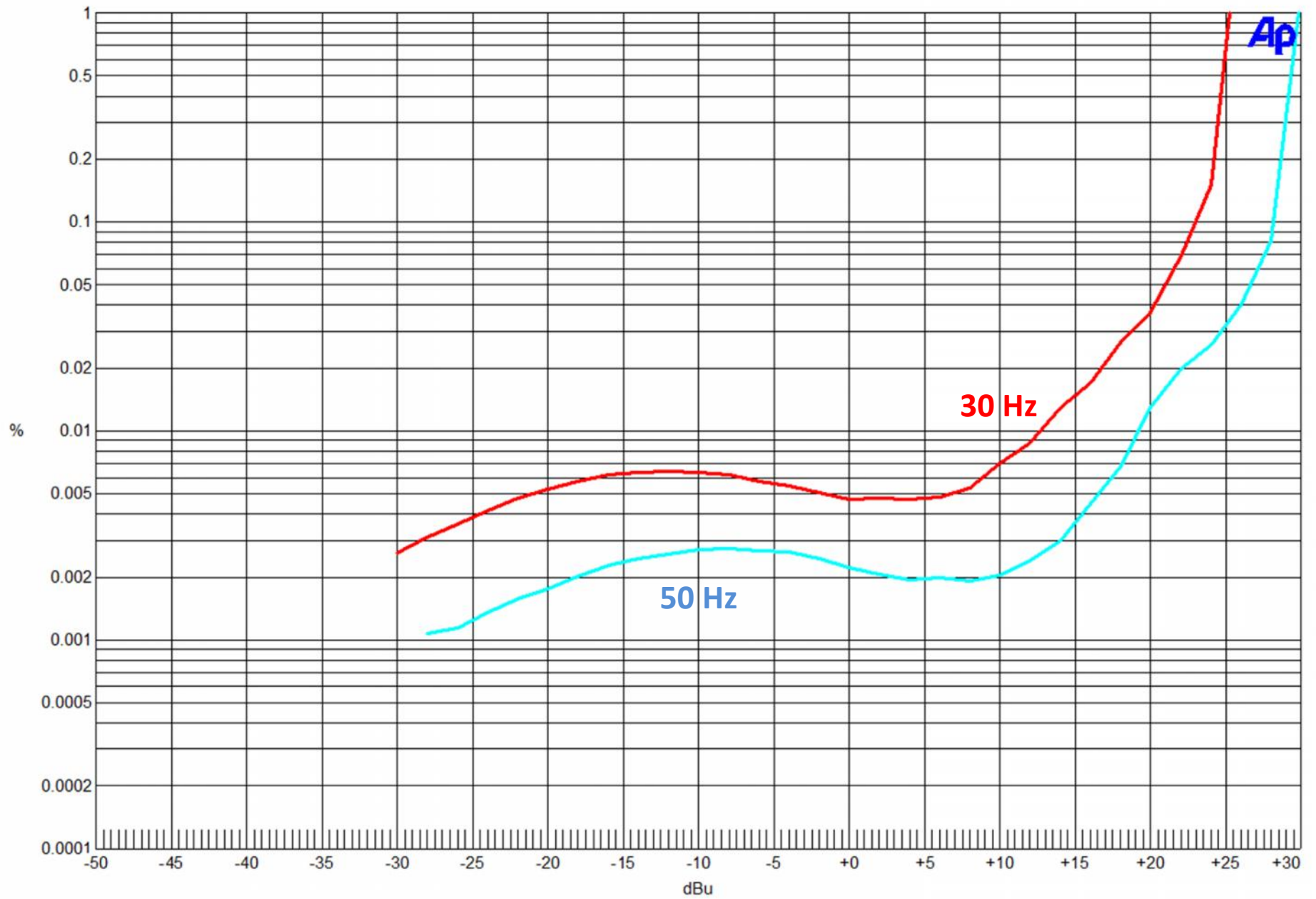JT-11-DM (HN) THD vs FREQUENCY: F = 30Hz, 50Hz, 100Hz, Rs = 150 Ohms




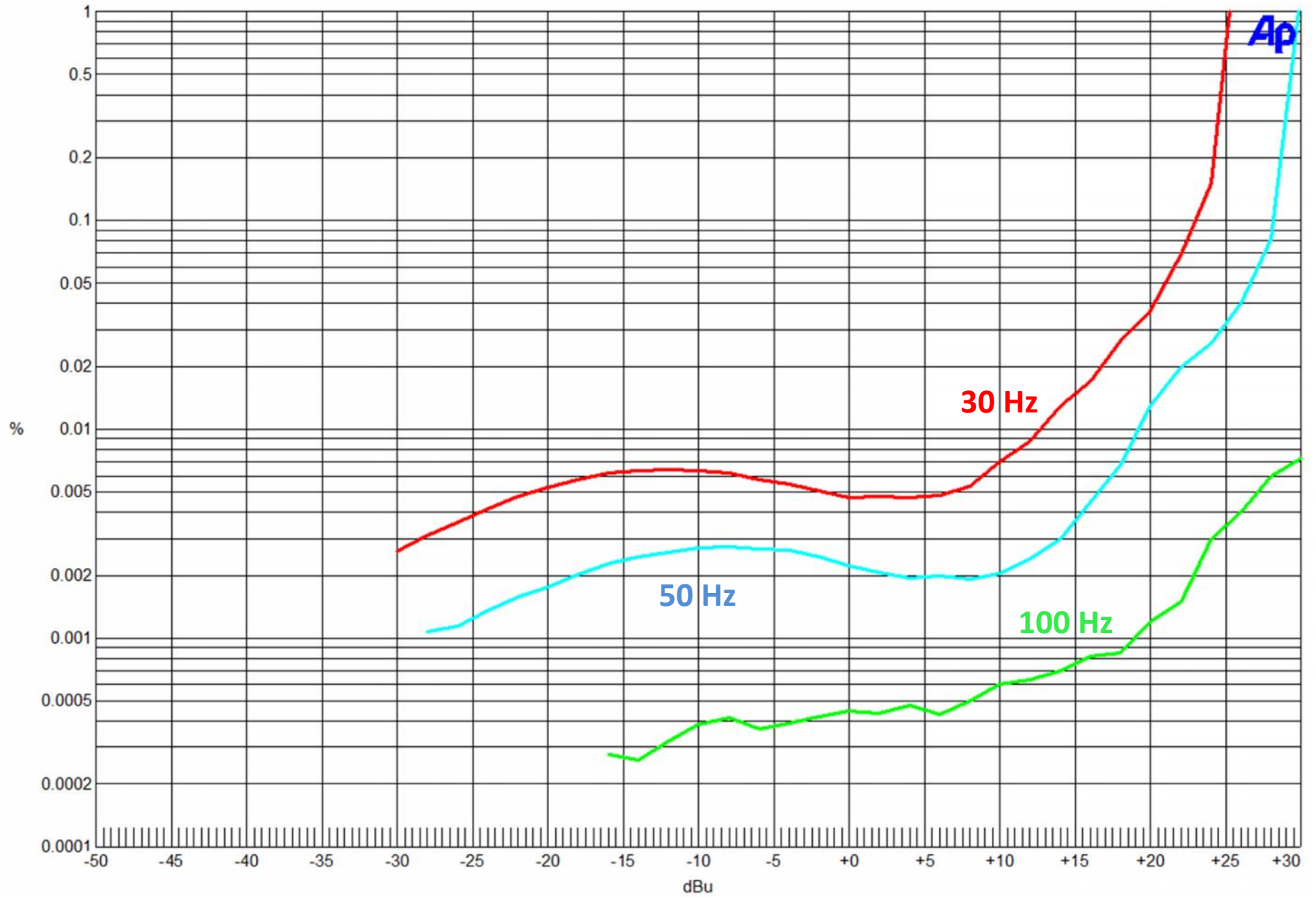JT-11-DM (HN) THD vs FREQUENCY: F = 30Hz, 50Hz, 100Hz, Rs = 150 Ohms



- THD increases with increasing Source Z.
- Output transformers should be driven with lowest possible Source Z.

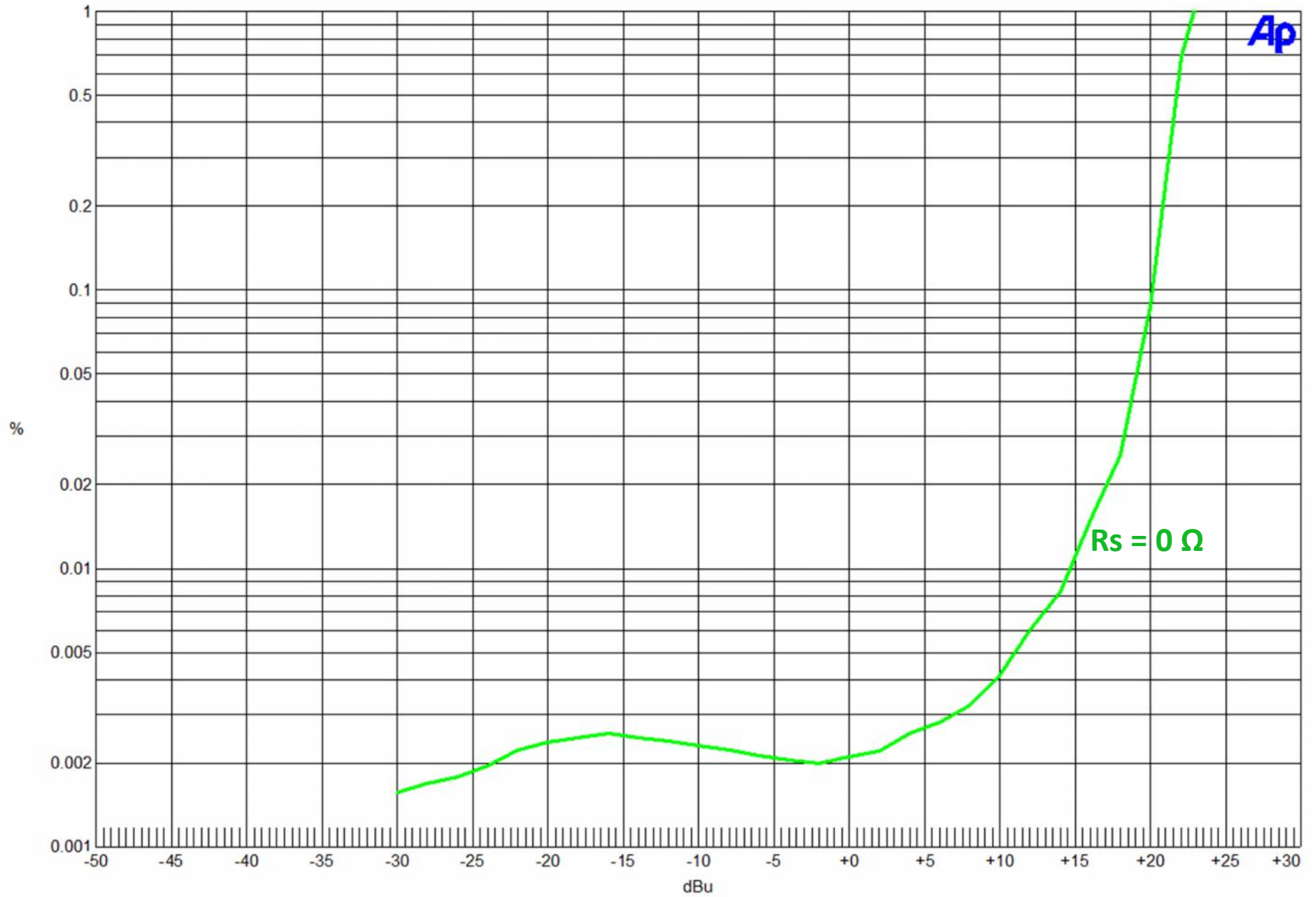
JT-11-DM (HN) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms




Ap

$R_s = 0 \Omega$

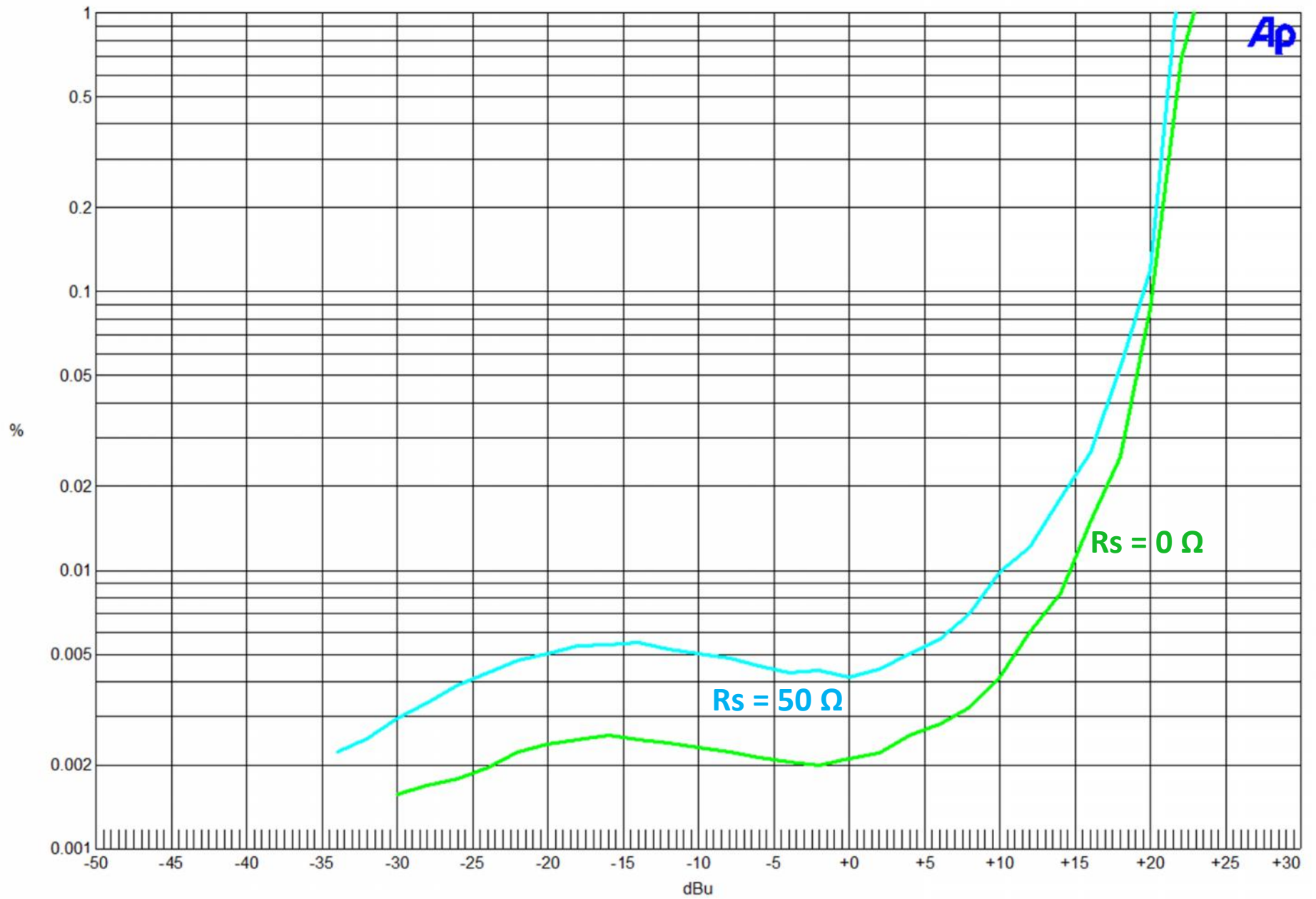JT-11-DM (HN) THD vs Level at Rs=0, 50, 150, 600 Ohms




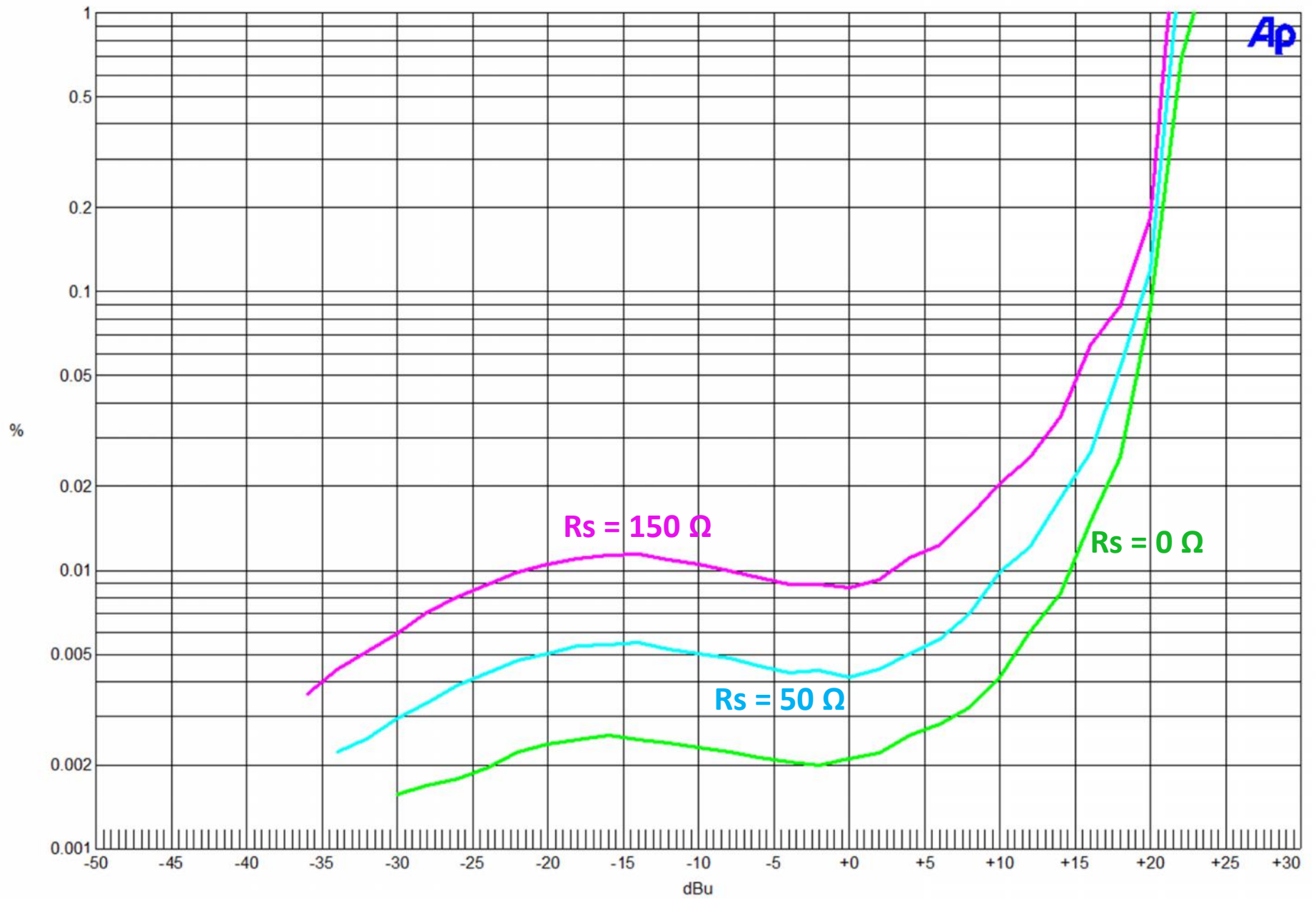JT-11-DM (HN) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms






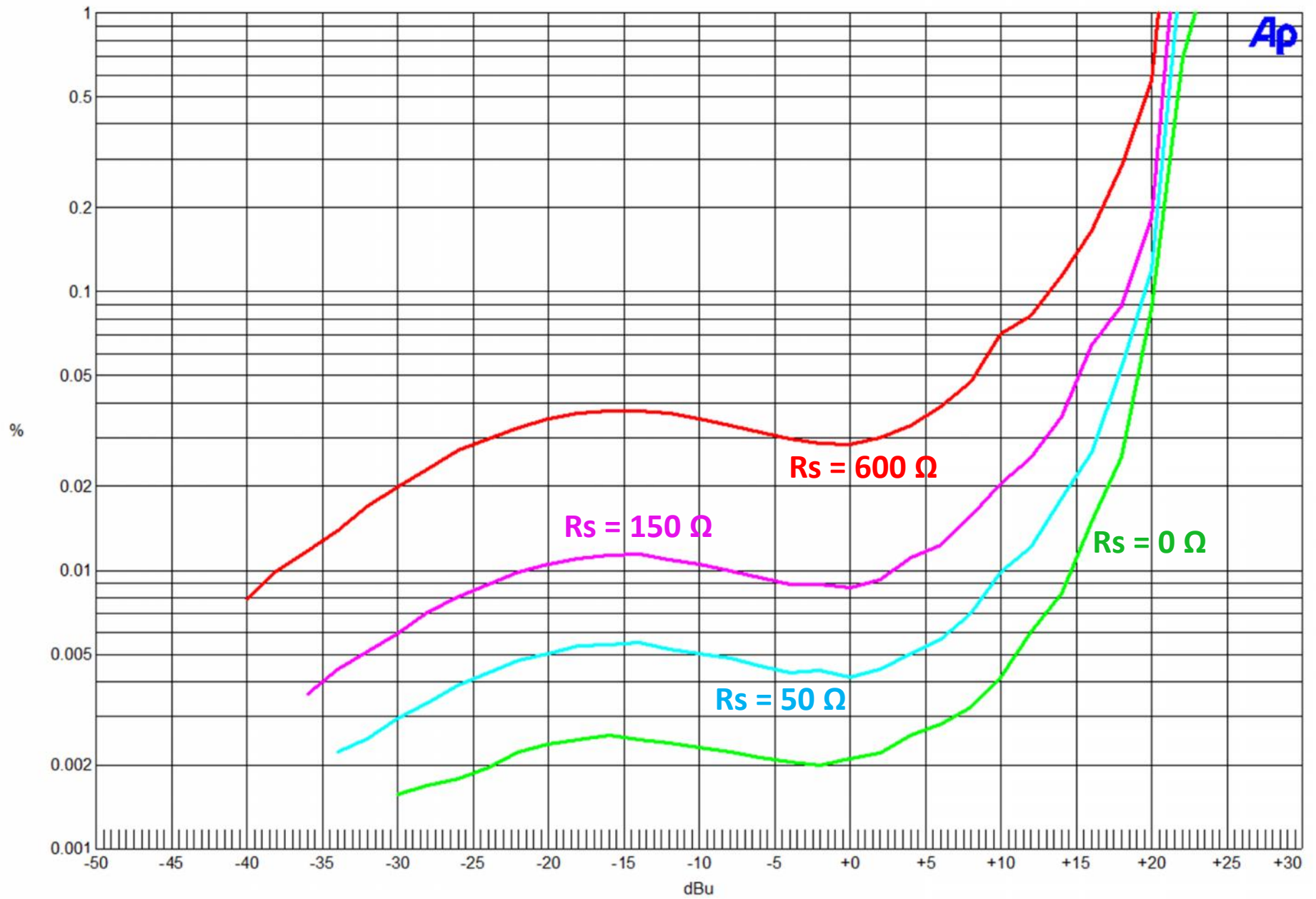JT-11-DM (HN) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms



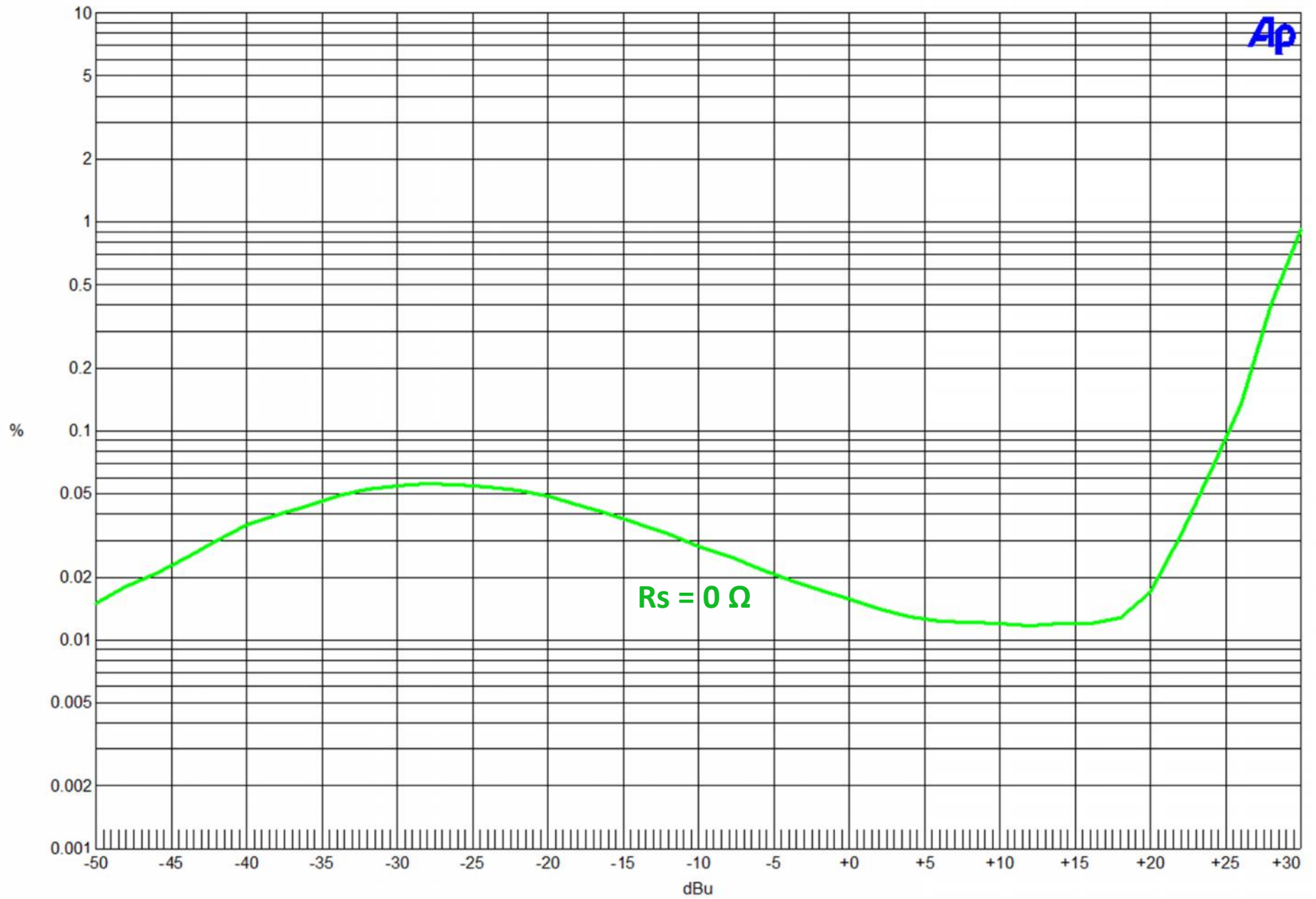
JT-11-DL (LN) THD vs Level at Rs=0, 50, 150, 600 Ohms




Ap

$R_s = 0 \Omega$

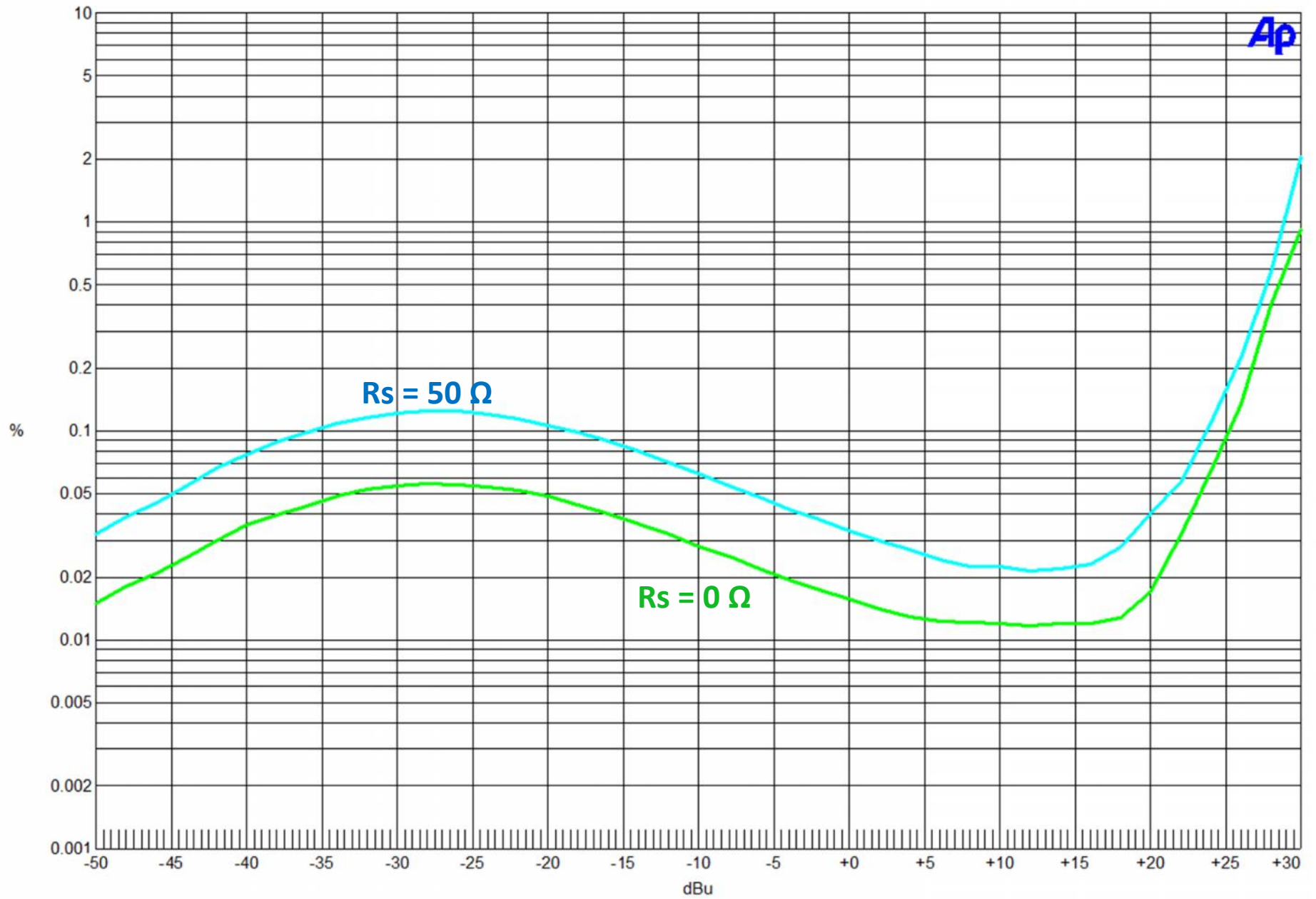
JT-11-DL (LN) THD vs Level at Rs=0, 50, 150, 600 Ohms



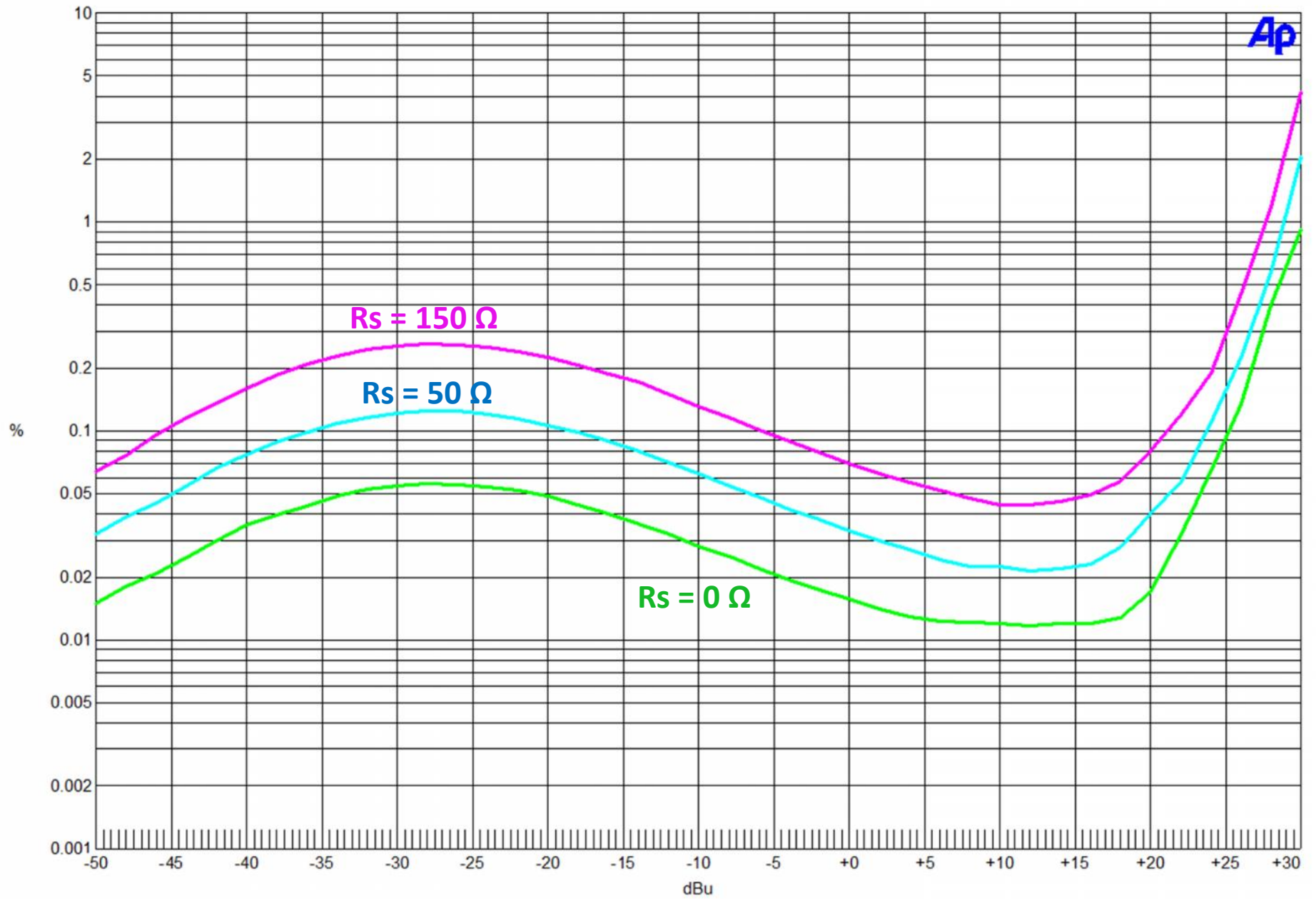
JT-11-DL (LN) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms



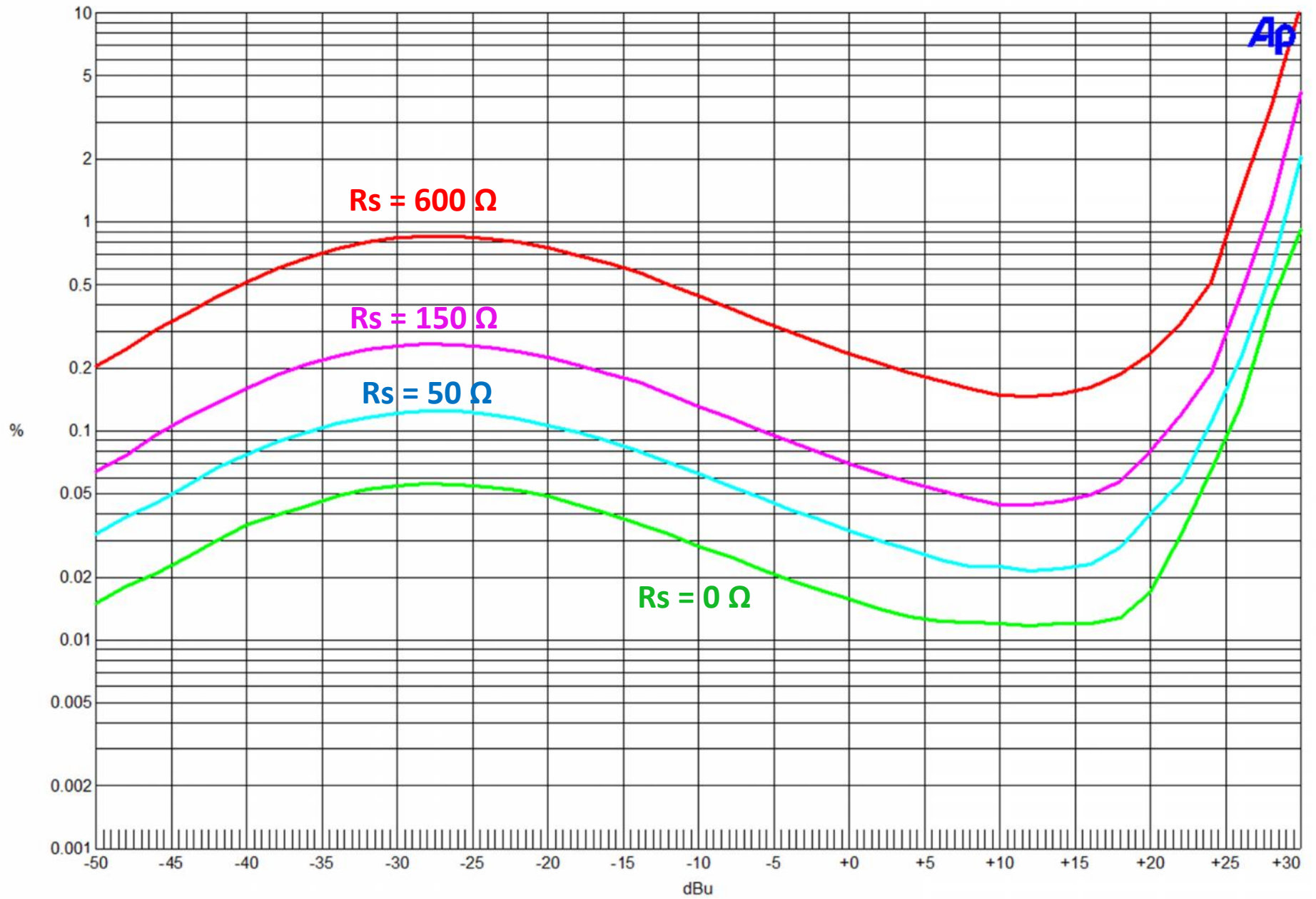JT-11-DL (LN) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms



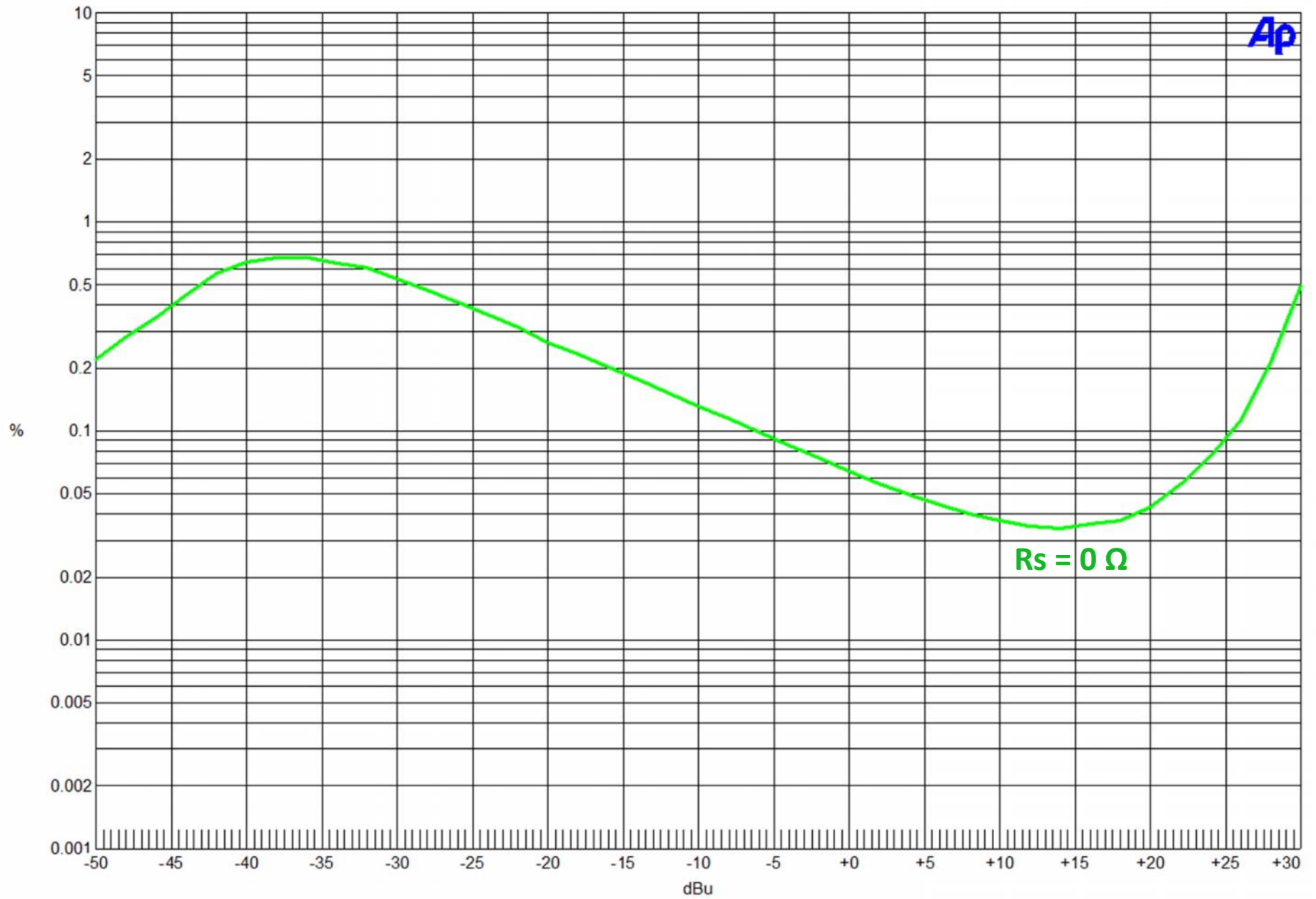
JT-11-D (M6 Steel) THD vs Level at Rs=0, 50, 150, 600 Ohms




Ap

Rs = 0 Ω

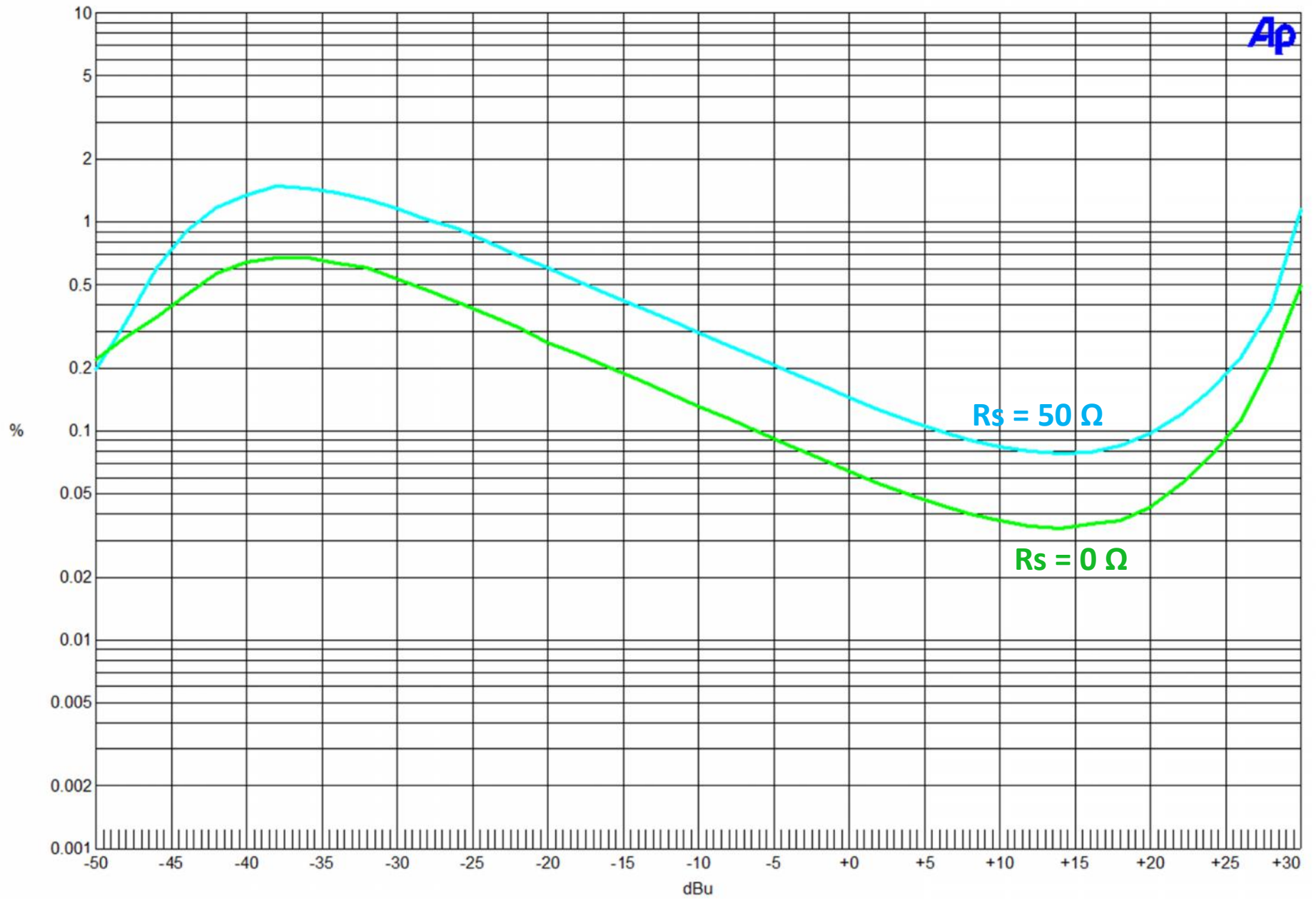JT-11-D (M6 Steel) THD vs Level at Rs=0, 50, 150, 600 Ohms




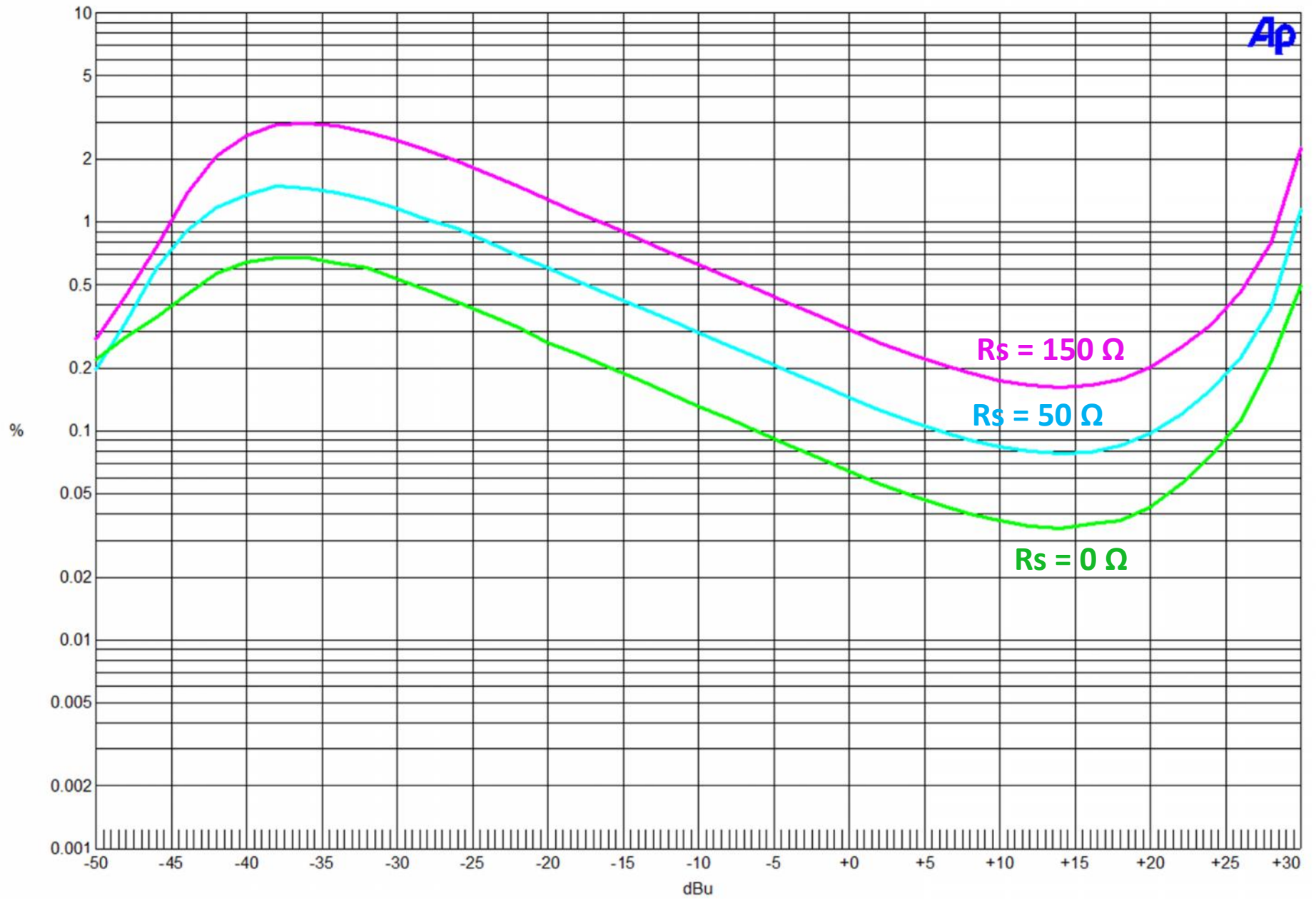JT-11-D (M6 Steel) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms






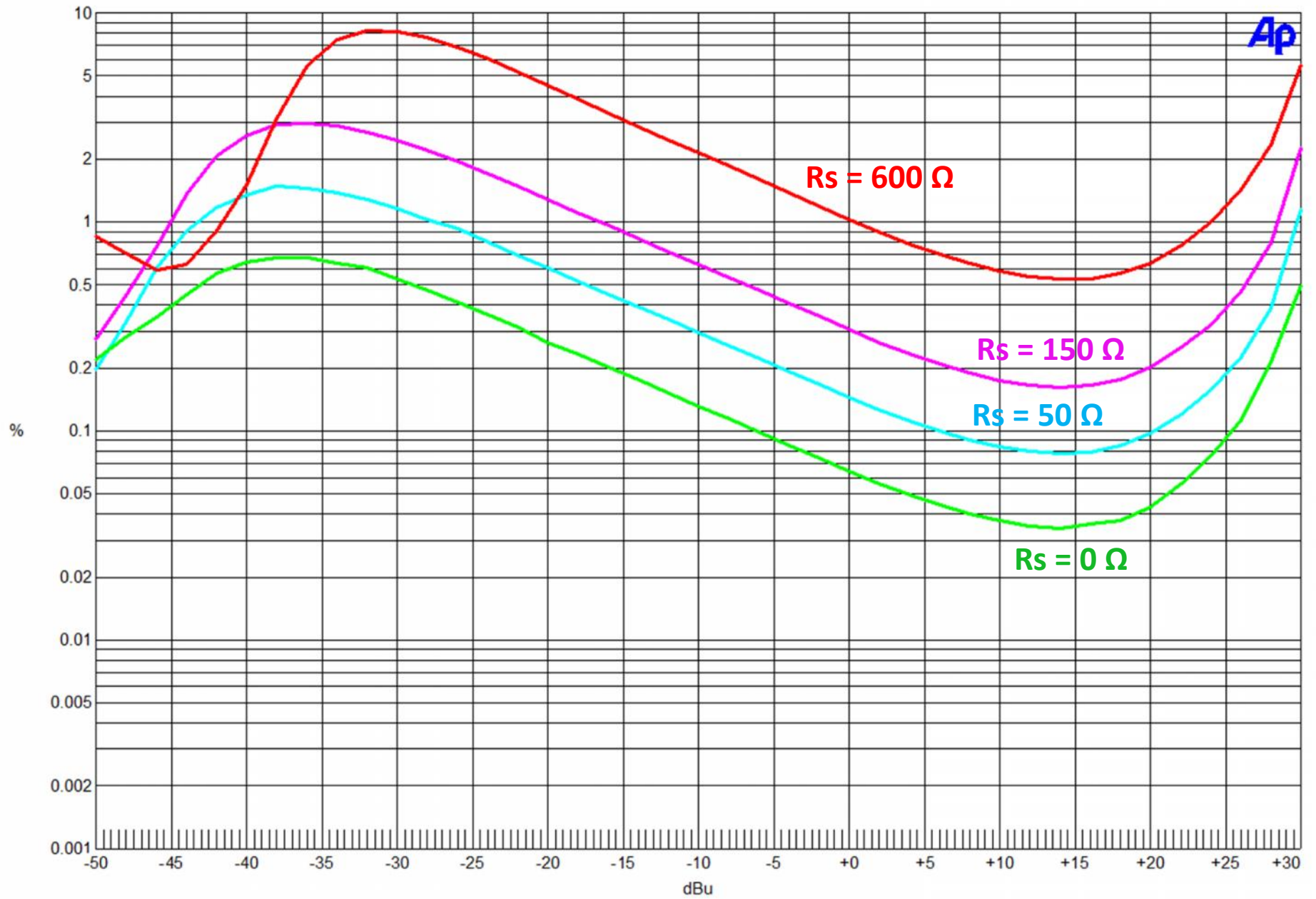JT-11-D (M6 Steel) THD vs Level at  $R_s=0, 50, 150, 600$  Ohms




# Steve's pick for Line Input Transformer

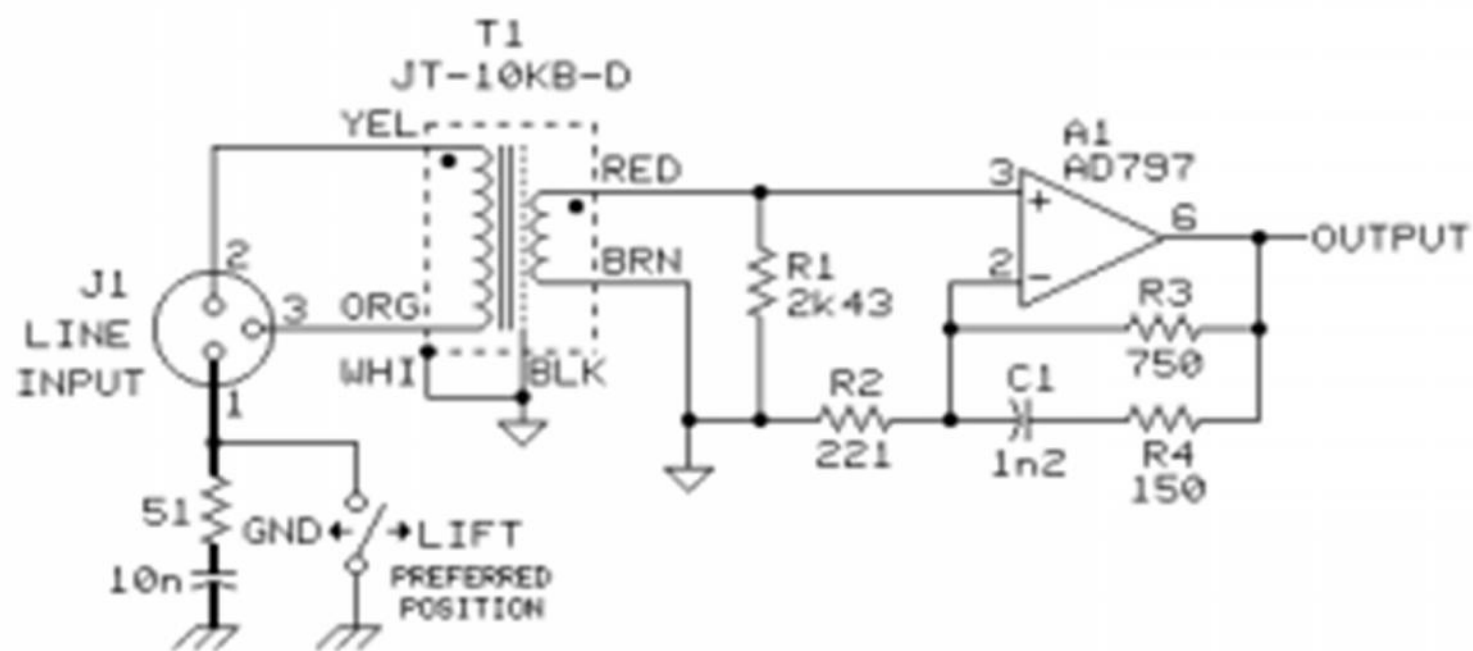- 4:1 step-down (JT-10KB-D) outperforms 1:1 input transformer (JT-11P-1) in line input applications.
- Higher CMRR: 120dB vs 107dB
- Lower THD: 0.015% vs 0.025% at 20 Hz
- Wider Bandwidth: 180kHz vs 95kHz
- Much lower secondary source Z allows for lower noise circuitry.
- 12dB step down allows more headroom at input and minimum 6dB gain in following amplifier.



LOW NOISE UNITY GAIN INPUT STAGE

### Typical Application

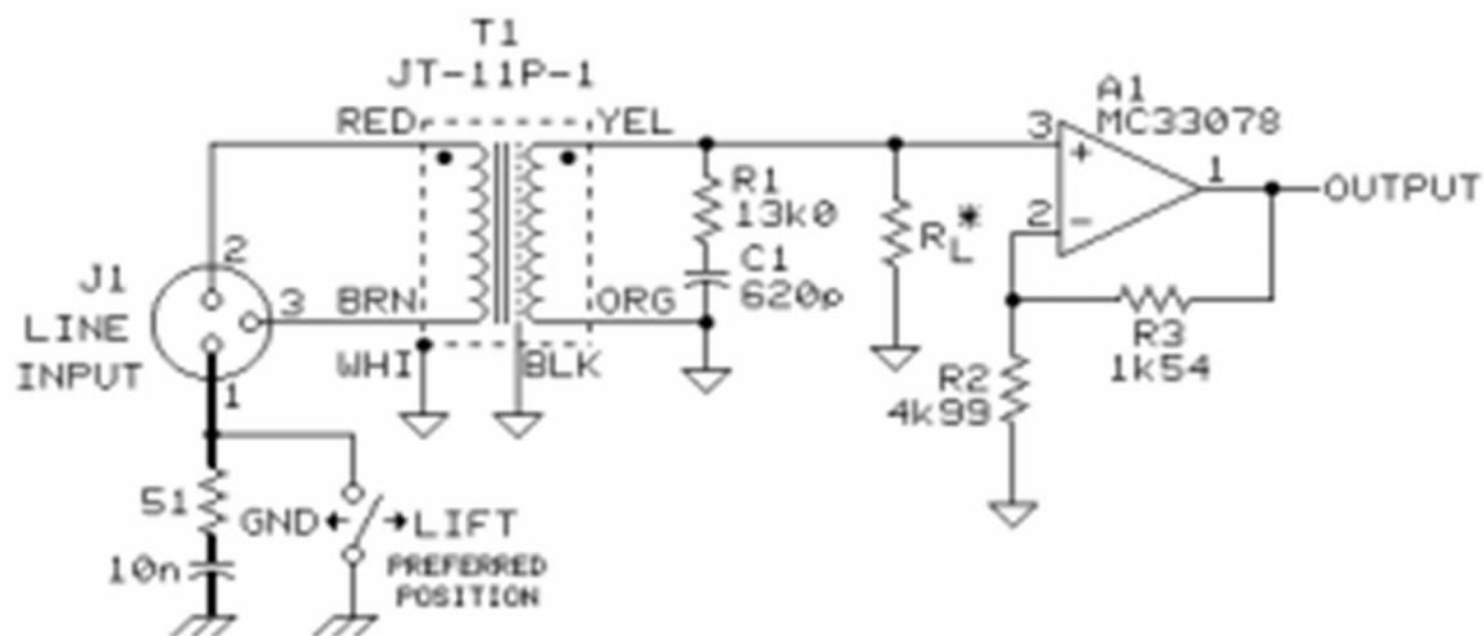

\*  $R_L$  MUST BE 10 k $\Omega$  OR GREATER

OMIT DAMPING NETWORK R1 AND C1 FOR  $R_L = 10$  k $\Omega$  ONLY


LOW NOISE UNITY GAIN INPUT STAGE

**Typical Application**

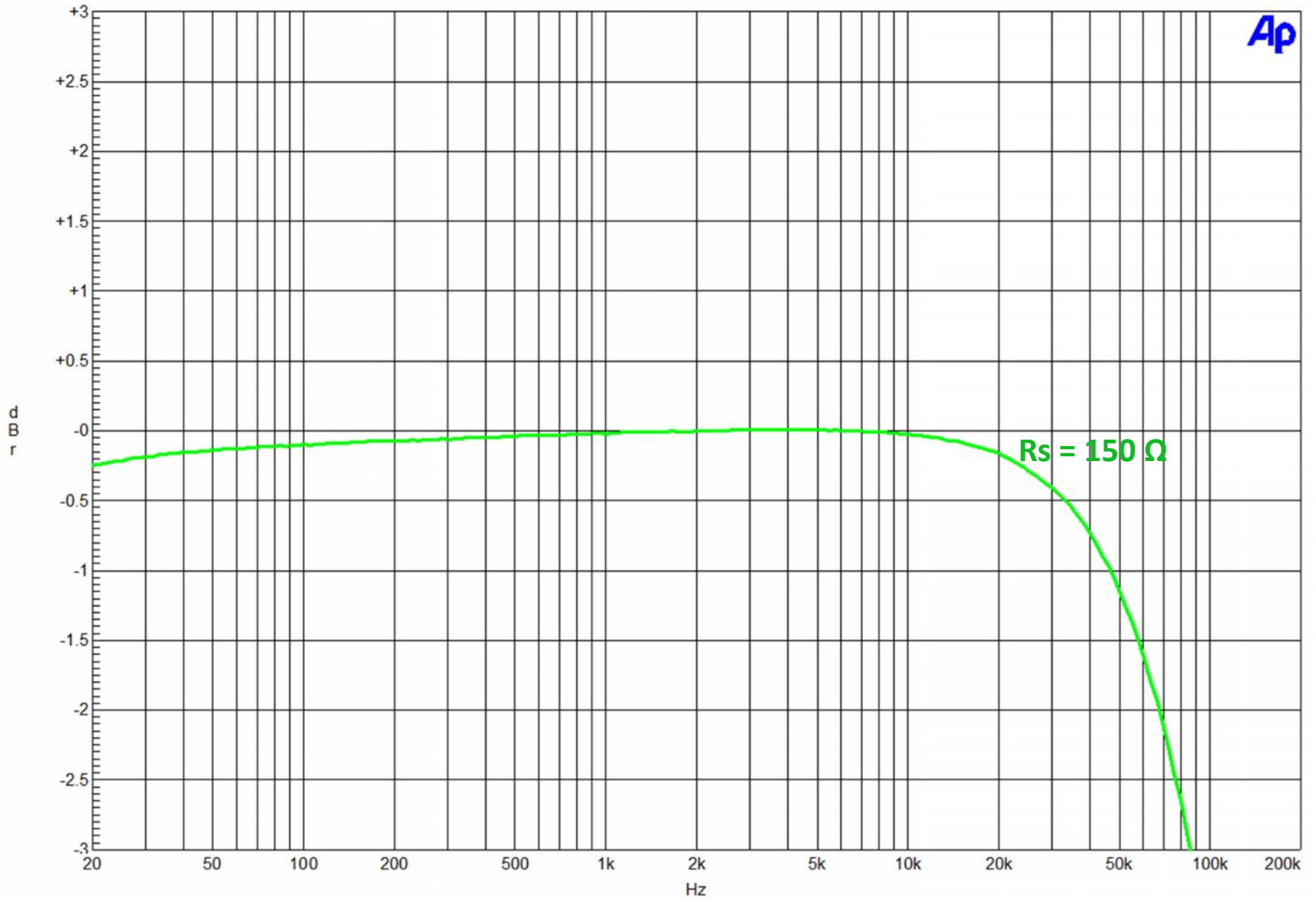
# Source Z and Mic Input Transformers

- Microphone output impedance (source Z to input transformer primary) can have a significant effect on the high frequency response and therefore the transient response of a transformer-balanced mic preamp.
- Source Z will have a lesser effect at low frequencies, with higher microphone output Z causing slightly more Low Frequency THD and more Low frequency roll-off.
- The source impedance effects are more pronounced in high-ratio (1:10) step-up mic transformers than in low ratio 1:2 step-up input transformers.
- Adding resistive build-outs to low-Z mics solves this problem completely. Hence “Low-Z mic” switch in the best transformer-based preamps.
- The recording engineer who knows the output Z of his microphones is in the position to get the best sound from his preamps.


JT-115K-E 1:10 Mic Input Transformer Frequency Response vs Source Z



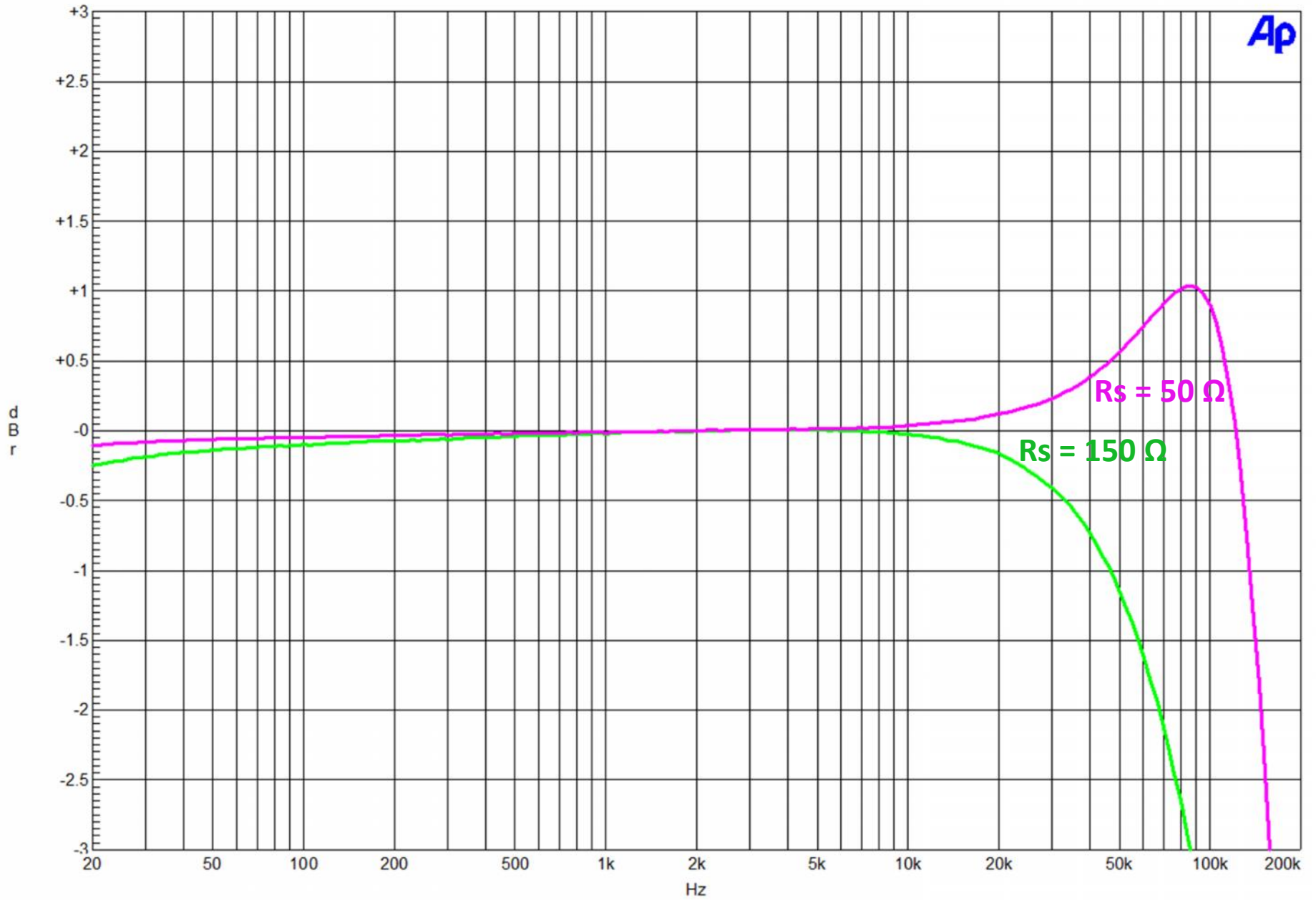JT-115K-E 1:10 Mic Input Transformer Frequency Response vs Source Z




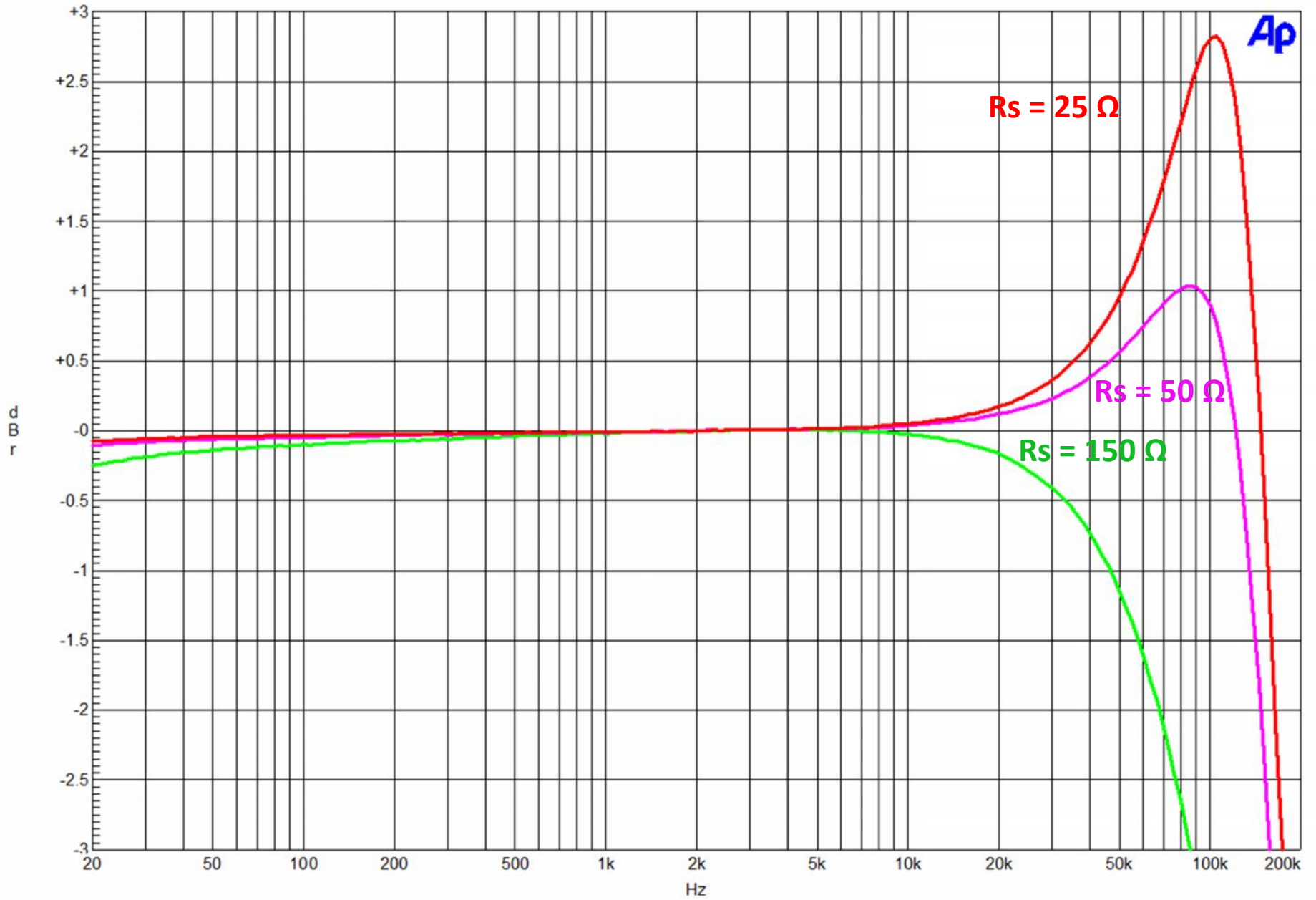JT-115K-E 1:10 Mic Input Transformer Frequency Response vs Source Z






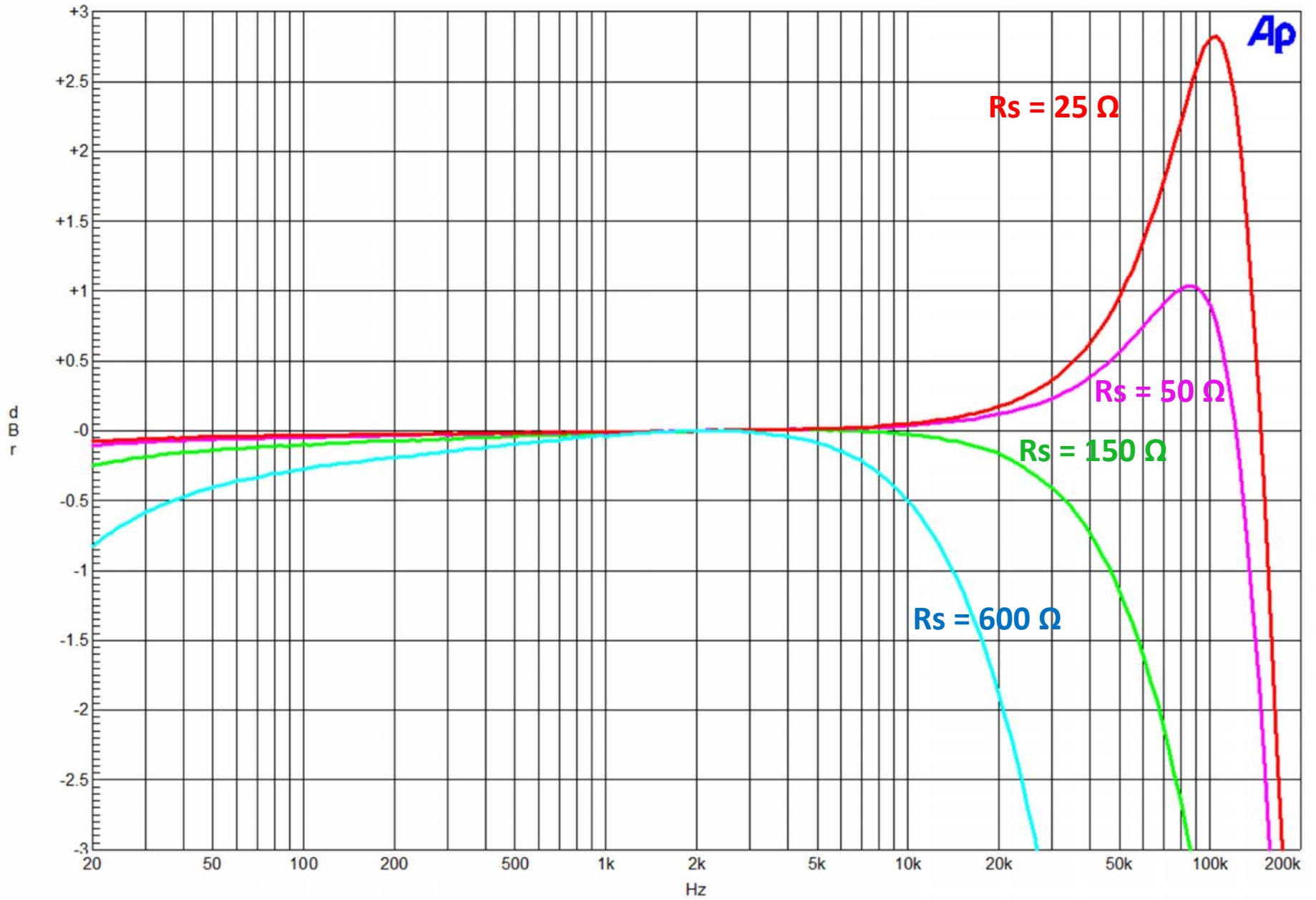
JT-115K-E 1:10 Mic Input Transformer Frequency Response vs Source Z



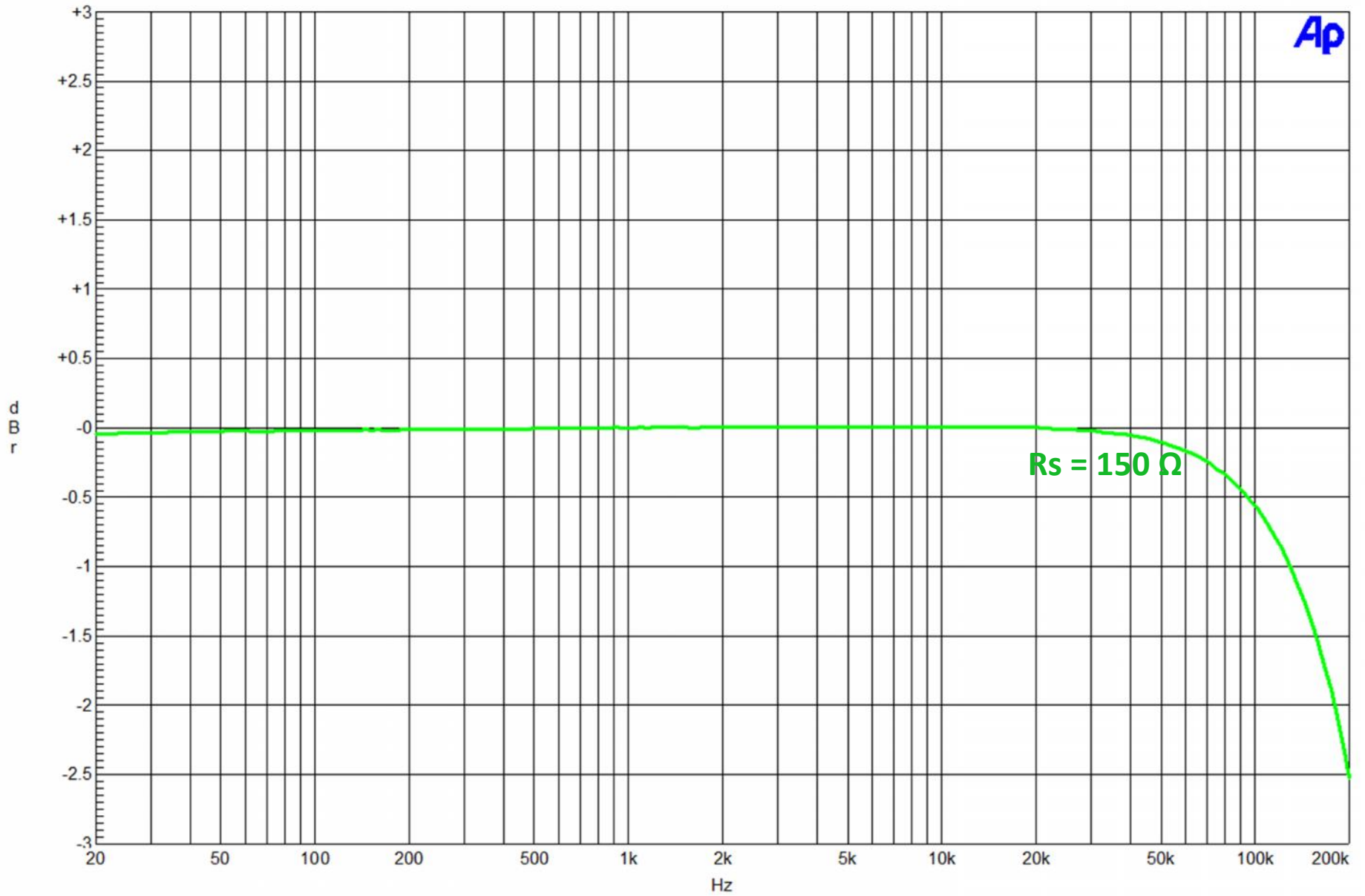
JT-16-A 1:2 Mic Input Transformer Frequency Response vs Source Z


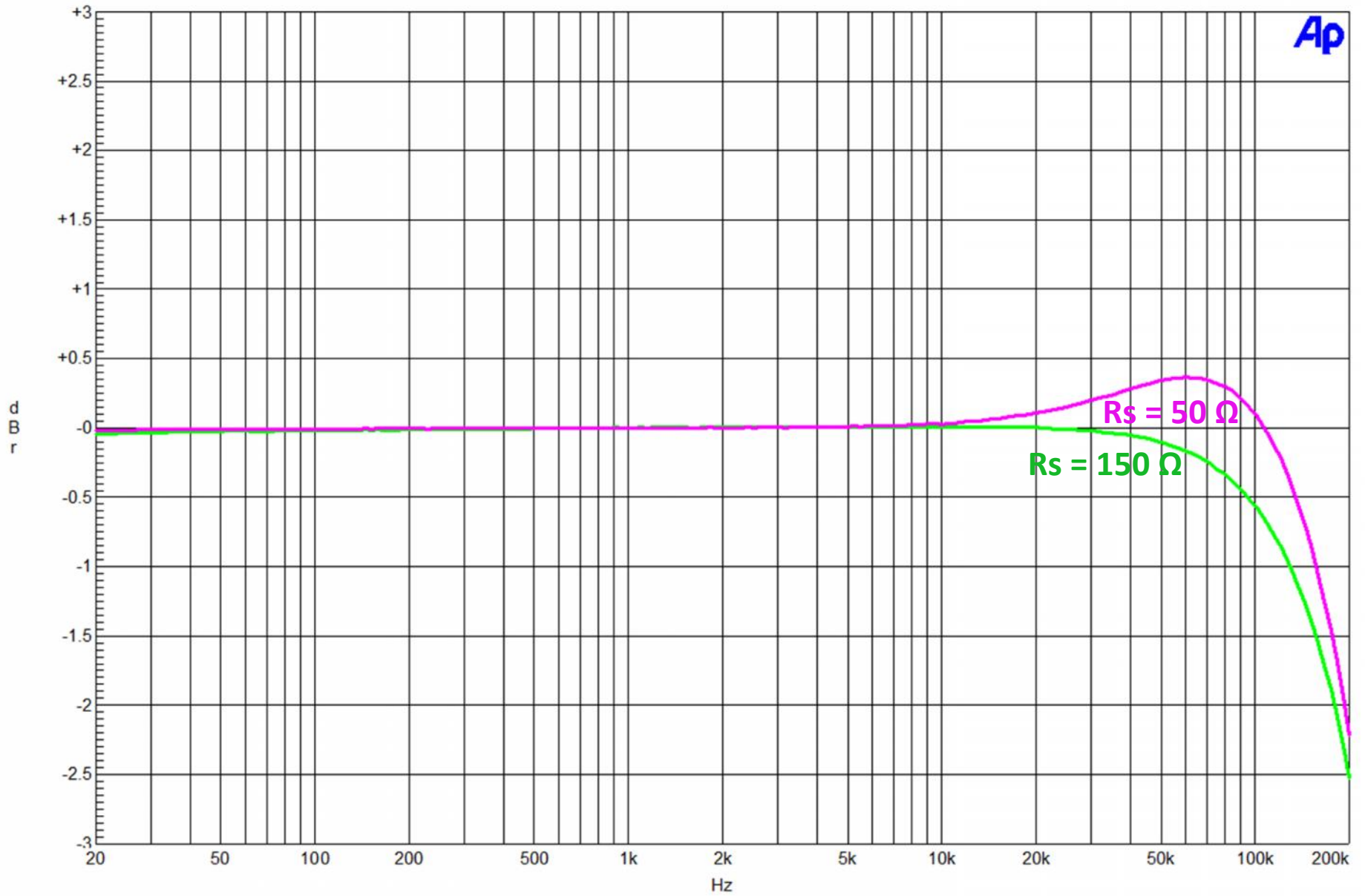
# JT-16-A 1:2 Mic Input Transformer Frequency Response vs Source Z


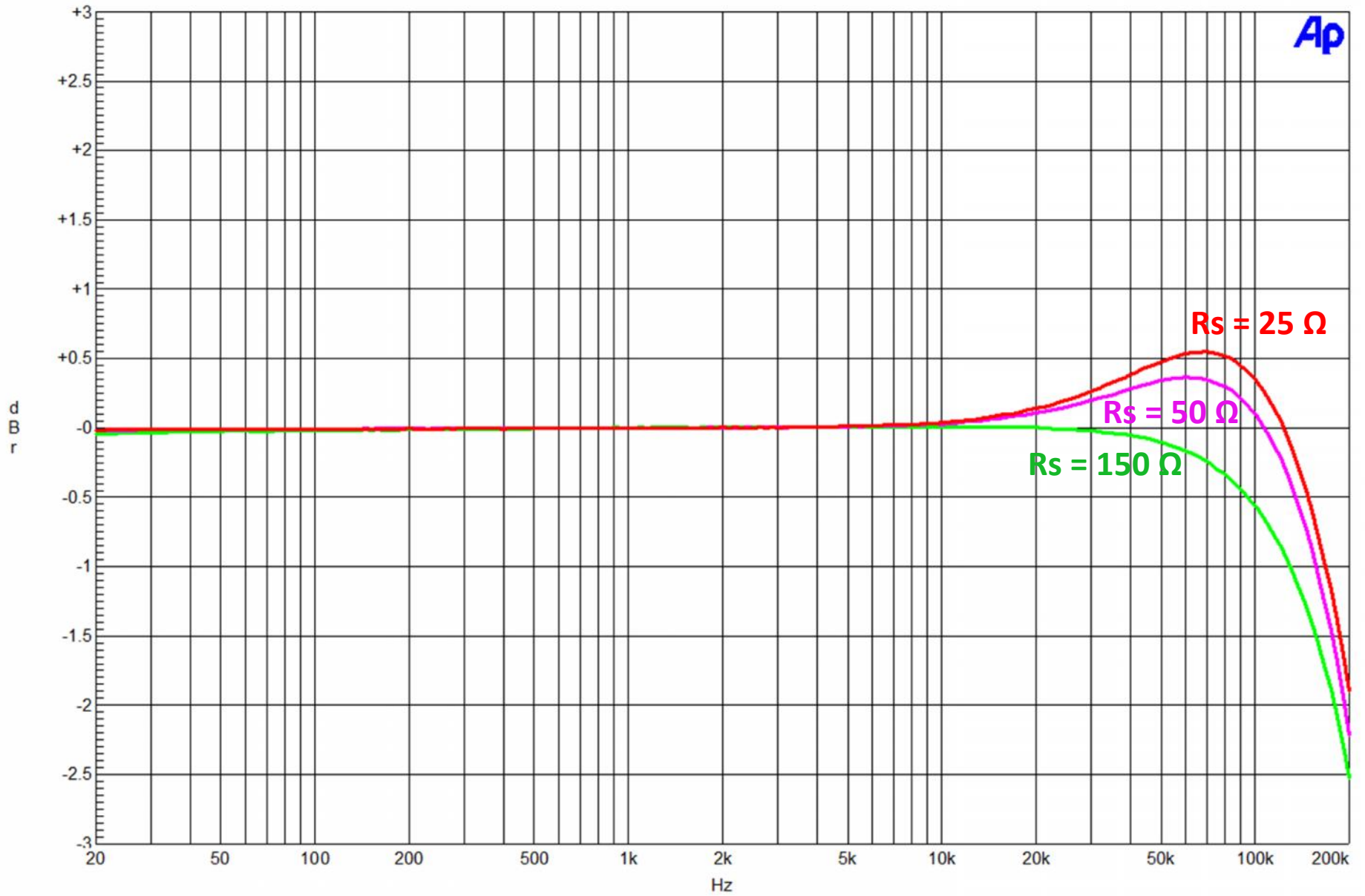
# JT-16-A 1:2 Mic Input Transformer Frequency Response vs Source Z



JT-16-A 1:2 Mic Input Transformer Frequency Response vs Source Z

